

معماری کامپیوتر

فصل سه

مدارهای محاسباتی



Computer Architecture

Chapter Three


Arithmetic Circuits



Copyright Notice

The slides of this lecture are adopted from:

 - ④ D. Patterson & J. Hennessey, “Computer Organization & Design, The Hardware/Software Interface”, 6th Ed., MK publishing, 2020




Outlines

- Shift
- Addition/Subtraction
 - Ripple-Carry Adders
 - Carry Look-ahead Adders
 - Carry-Select Adders
- Multiplication
 - Shift-Add Multiplier
 - Combinational Multiplier
 - Carry-Save Adder Multiplier
- Division
- Floating Point
 - Representation
 - Arithmetic




Shift Registers

Sequential Circuits

 


Barrel Shifter

Combinational Circuits

 


Barrel Shifter

 
- Shift an **optional** no of bits
- With a sequence of multiplexers
 - each shifting a word by 2^k bit positions for different values of k



Mux Implementation

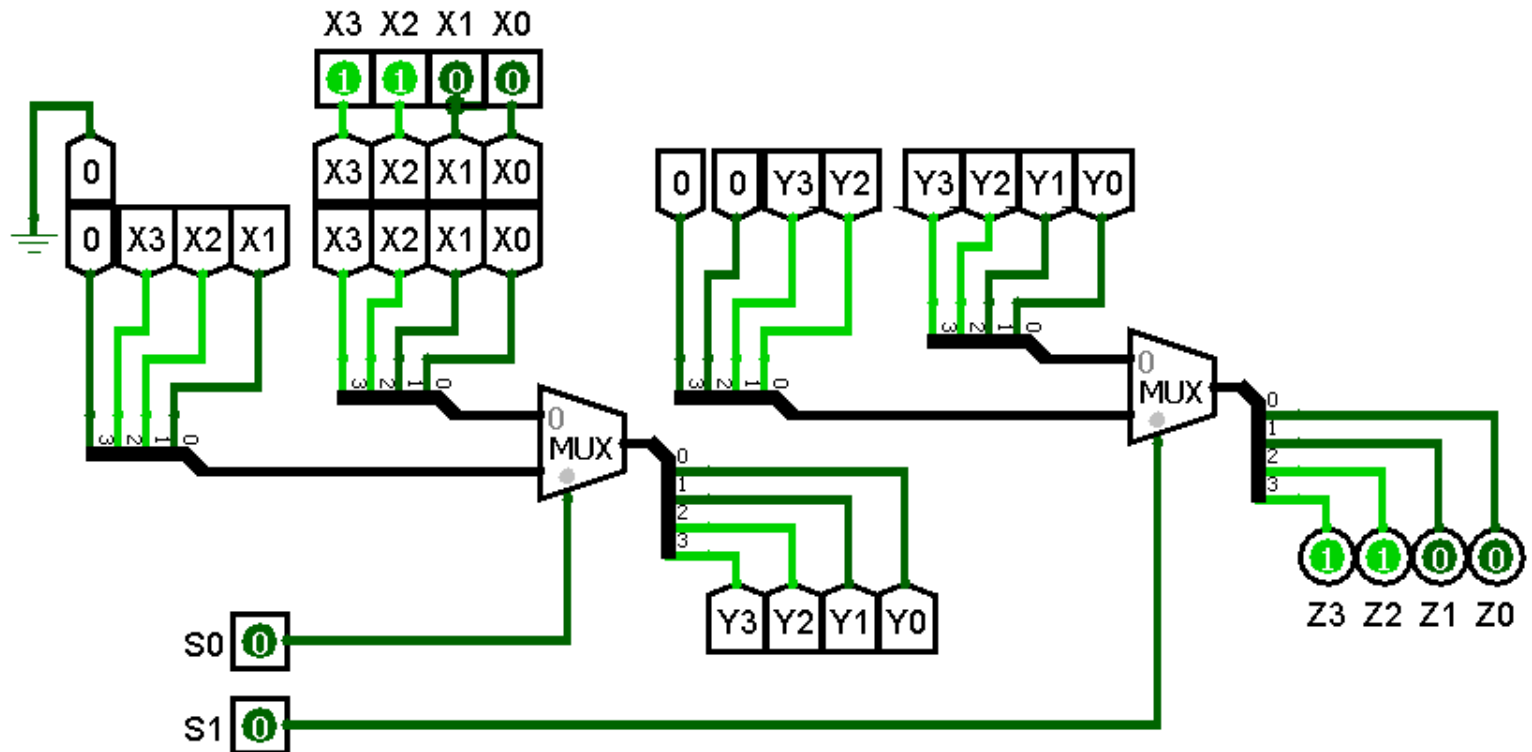

Crossbar (Circular) Barrel Shifter

 

Outlines

- Shift
- Addition/Subtraction
 - Ripple-Carry Adders
 - Carry Look-ahead Adders
 - Carry-Select Adders
- Multiplication
 - Shift-Add Multiplier
 - Combinational Multiplier
 - Carry-Save Adder Multiplier
- Division
- Floating Point
 - Representation
 - Arithmetic



Integer Addition / Subtraction

$$\begin{array}{r}
 0000000000000000 \\
 000000000001000000 + \\
 00000000000101010 \\
 \hline
 000000000001101010
 \end{array}$$

$$\begin{array}{r}
 64 \\
 + 42 \\
 \hline
 106
 \end{array}$$

$$\begin{array}{r}
 1111111111000000 \\
 000000000001000000 + \\
 1111111111010110 \\
 \hline
 0000000000010110
 \end{array}$$

$$\begin{array}{r}
 64 \\
 - 42 \\
 \hline
 22
 \end{array}$$

2's
complement




Overflow Conditions for Add/Sub

Operation	Operand A	Operand B	Result indicating overflow
$A + B$	≥ 0	≥ 0	< 0
$A + B$	< 0	< 0	≥ 0
$A - B$	≥ 0	< 0	< 0
$A - B$	< 0	≥ 0	≥ 0

- While adding signed numbers, an overflow occurs when
 - Both operands have the same sign,
 - but the result has the opposite sign
- the carry into and out of the MSB differ



One-bit Full Adder

 

Input and output specification for a 1-bit adder


Inputs			Outputs		Comments
a	b	CarryIn	CarryOut	Sum	
0	0	0	0	0	$0 + 0 + 0 = 00_{\text{two}}$
0	0	1	0	1	$0 + 0 + 1 = 01_{\text{two}}$
0	1	0	0	1	$0 + 1 + 0 = 01_{\text{two}}$
0	1	1	1	0	$0 + 1 + 1 = 10_{\text{two}}$
1	0	0	0	1	$1 + 0 + 0 = 01_{\text{two}}$
1	0	1	1	0	$1 + 0 + 1 = 10_{\text{two}}$
1	1	0	1	0	$1 + 1 + 0 = 10_{\text{two}}$
1	1	1	1	1	$1 + 1 + 1 = 11_{\text{two}}$

$$\text{Sum} = a \oplus b \oplus \text{CarryIn}$$

$$\text{CarryOut} = a.b + a.\text{CarryIn} + b.\text{CarryIn}$$




Ripple-Carry Adder

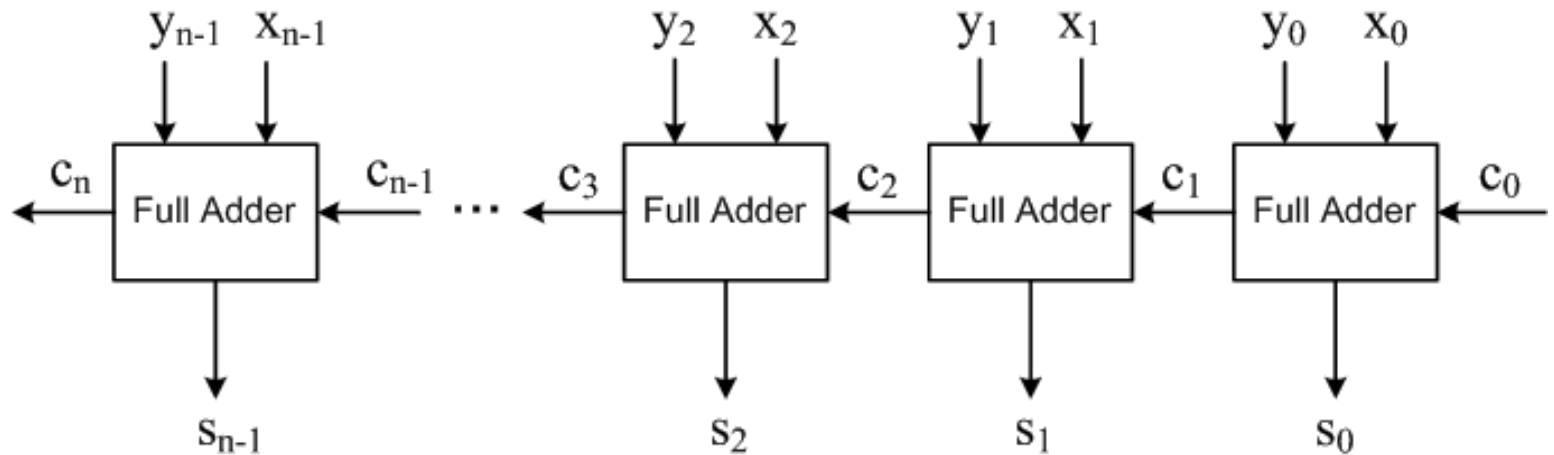


Analysis (n-bit Ripple-Carry Adder)

 - **Cost:** $O(n)$
 - $n \times \text{F.A.}$
- Critical Path **Delay:** $O(n)$
 - $n \times D_{\text{FA}} = 2n \times D_{\text{gate}}$



Carry Look-Ahead Adders

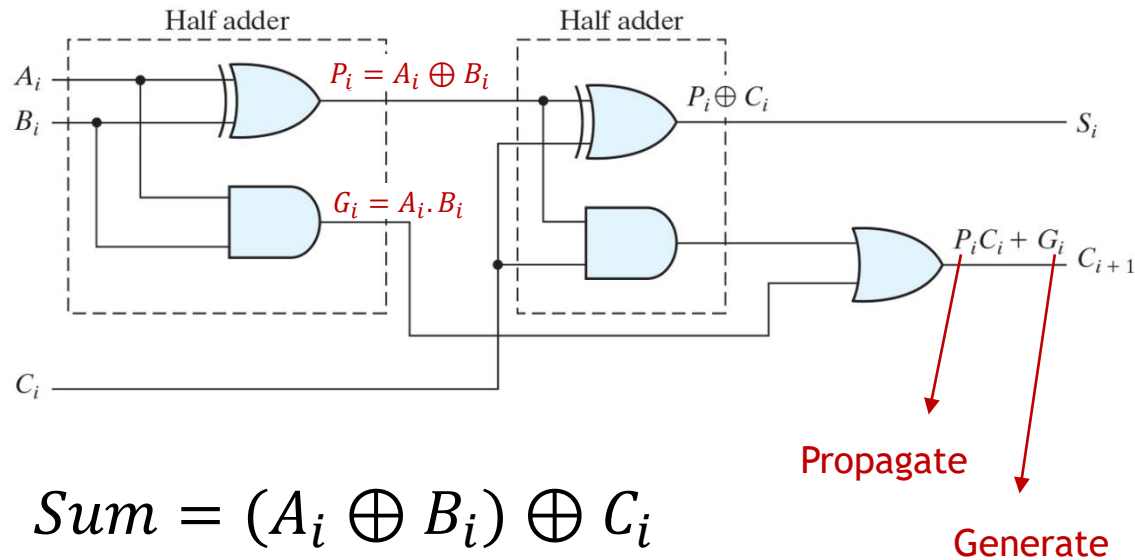Is there any way to calculate the final carry-out in just two levels of logic?



$$Sum = (A_i \oplus B_i) \oplus C_i$$

$$C_{i+1} = A_i B_i + C_i (A_i \oplus B_i)$$



Carry Look-Ahead Adders

Is there any way to calculate the final carry-out in just two levels of logic?

$$c_1 = g_0 + p_0 \cdot c_0$$

$$c_2 = g_1 + p_1 \cdot g_0 + p_1 \cdot p_0 \cdot c_0$$

$$c_3 = g_2 + p_2 \cdot g_1 + p_2 \cdot p_1 \cdot g_0 + p_2 \cdot p_1 \cdot p_0 \cdot c_0$$

$$c_4 = g_3 + p_3 \cdot g_2 + p_3 \cdot p_2 \cdot g_1 + p_3 \cdot p_2 \cdot p_1 \cdot g_0 + p_3 \cdot p_2 \cdot p_1 \cdot p_0 \cdot c_0$$




1st Level of Abstraction

$$c_1 = g_0 + p_0 \cdot c_0$$

$$c_2 = g_1 + p_1 \cdot g_0 + p_1 \cdot p_0 \cdot c_0$$

$$c_3 = g_2 + p_2 \cdot g_1 + p_2 \cdot p_1 \cdot g_0 + p_2 \cdot p_1 \cdot p_0 \cdot c_0$$
 
$$c_4 = g_3 + p_3 \cdot g_2 + p_3 \cdot p_2 \cdot g_1 + p_3 \cdot p_2 \cdot p_1 \cdot g_0 + p_3 \cdot p_2 \cdot p_1 \cdot p_0 \cdot c_0$$



2-Level Abstraction

$$c_4 = \underbrace{(g_3 + p_3 \cdot g_2 + p_3 \cdot p_2 \cdot g_1 + p_3 \cdot p_2 \cdot p_1 \cdot g_0)}_{G0} + \underbrace{(p_3 \cdot p_2 \cdot p_1 \cdot p_0)}_{P0} \cdot \underbrace{c_0}_{C0}$$


\downarrow \downarrow \downarrow
C1 **G0** **P0** **C0**

$$C1 = G0 + P0 \cdot C0$$

$$C2 = G1 + P1 \cdot C1$$

$$C3 = G2 + P2 \cdot C2$$

$$C4 = G3 + P3 \cdot C3$$

 

2-Level Abstraction

$$C1 = G0 + P0.C0$$

$$C2 = G1 + P1.G0 + P1.P0.C0$$

$$C3 = G2 + P2.G1 + P2.P1.G0 + P2.P1.P0.C0$$

$$C4 = G3 + P3.G2 + P3.P2.G1 + P3.P2.P1.G0 + P3.P2.P1.P0.C0$$

$$P0 = p_3 \cdot p_2 \cdot p_1 \cdot p_0$$

$$P1 = p_7 \cdot p_6 \cdot p_5 \cdot p_4$$

$$P2 = p_{11} \cdot p_{10} \cdot p_9 \cdot p_8$$


$$P3 = p_{15} \cdot p_{14} \cdot p_{13} \cdot p_{12}$$

$$G0 = g_3 + p_3 \cdot g_2 + p_3 \cdot p_2 \cdot g_1 + p_3 \cdot p_2 \cdot p_1 \cdot g_0$$

$$G1 = g_7 + p_7 \cdot g_6 + p_7 \cdot p_6 \cdot g_5 + p_7 \cdot p_6 \cdot p_5 \cdot g_4$$

$$G2 = g_{11} + p_{11} \cdot g_{10} + p_{11} \cdot p_{10} \cdot g_9 + p_{11} \cdot p_{10} \cdot p_9 \cdot g_8$$
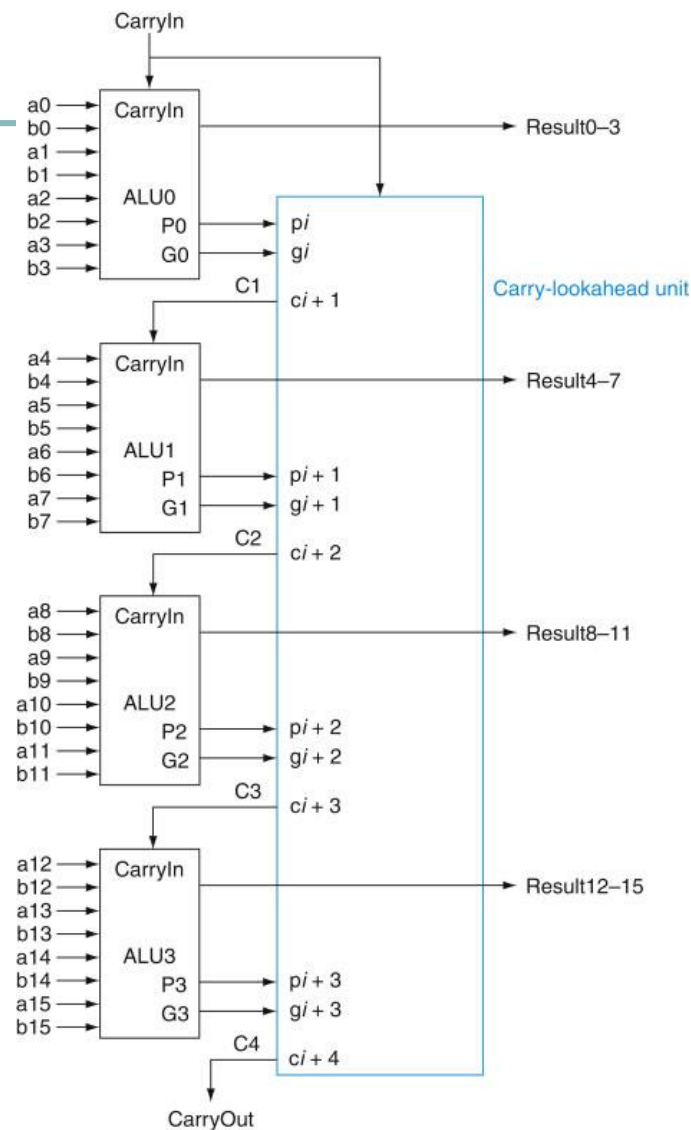
$$G3 = g_{15} + p_{15} \cdot g_{14} + p_{15} \cdot p_{14} \cdot g_{13} + p_{15} \cdot p_{14} \cdot p_{13} \cdot g_{12}$$



Analysis (16-bit 2-level CLA)

- **Cost:**
 - $O(n^2)$
- **Critical Path Delay:**
 - 1 D_{gate} for $a_i, b_i \rightarrow g_i, p_i$
 - 2 D_{gate} for $g_i, p_i \rightarrow G_i, P_i$
 - 2 D_{gate} for $G_i, P_i \rightarrow C_i$
 - 2 D_{gate} for $C_i \rightarrow c_i$
 - 1 D_{gate} for $c_i \rightarrow S_i$



Check Yourself

- What is the relative performance of a ripple carry 8-bit add vs. a 64-bit add using carry look-ahead logic?
 - A 64-bit carry-lookahead adder is faster
 - They are about the same speed, since 64-bit adds need more levels of logic in the 16-bit adder
 - 8-bit adds are faster than 64 bits, even with carry look-ahead




Carry-Select Adders


- K stages of n/K bit ripple carry adders can be used to add n -bit numbers
- The numbers are added **twice** in each stage
 - One time assuming carry-in is **zero**
 - Other time assuming the carry-in is **one**
- The correct sum and carry-out is **selected** by a multiplexer, when the correct carry-in is known




Building Block

 

Uniform-Sized Adder

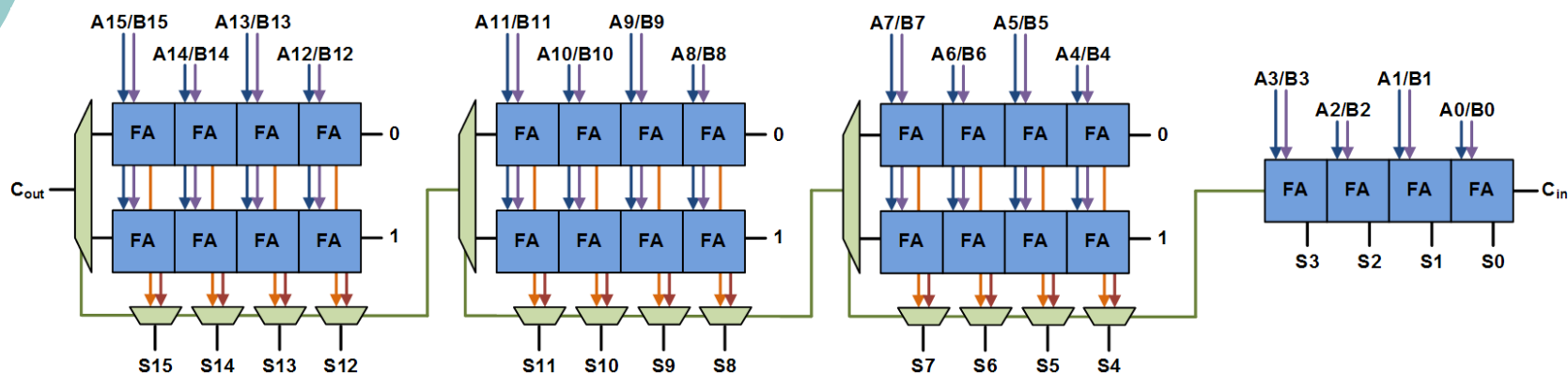


Variable-Sized Adder

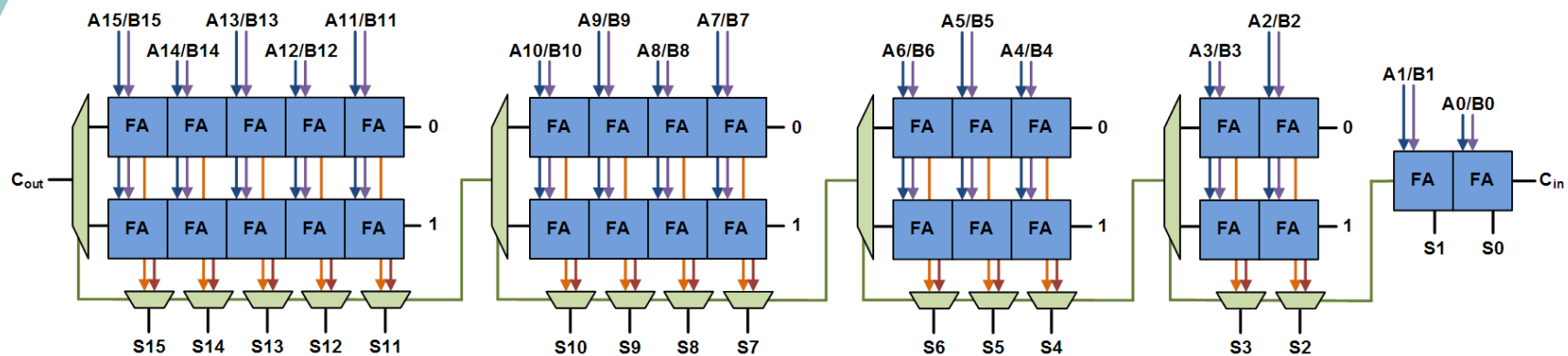

Analysis (n-bit k-stage CSA)

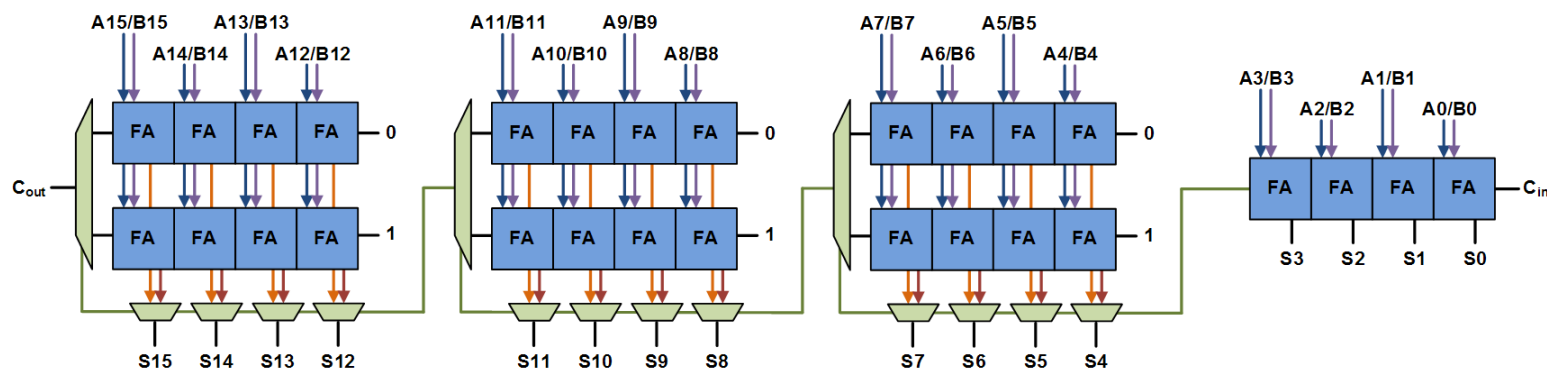- **Cost:**
 - Full Adders: $n/K \times (2K-1)$
 - Mux: $(K-1)(n/K+1)$
- **Critical Path Delay:**
 - $n/K \times D_{FA} + (K-1) \times D_{MUX}$




Outlines


- Shift
- Addition/Subtraction
 - Ripple-Carry Adders
 - Carry Look-ahead Adders
 - Carry-Select Adders
- Multiplication
 - Shift-Add Multiplier
 - Combinational Multiplier
 - Carry-Save Adder Multiplier
- Division
- Floating Point
 - Representation
 - Arithmetic




Multiplication Approach (1st ver)

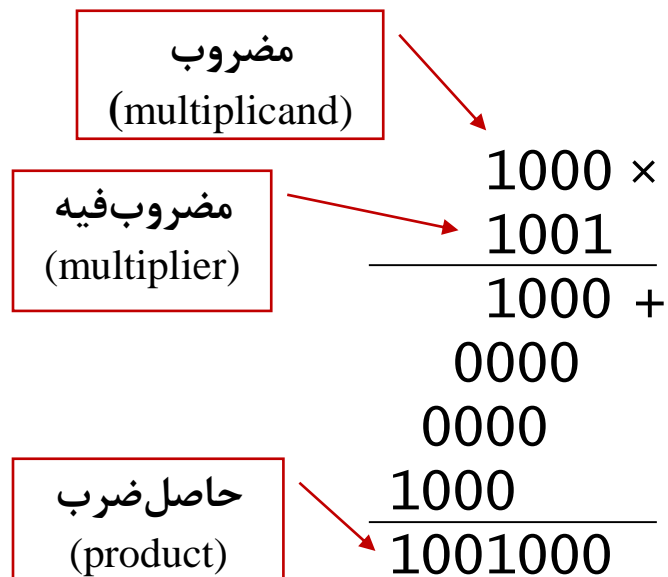

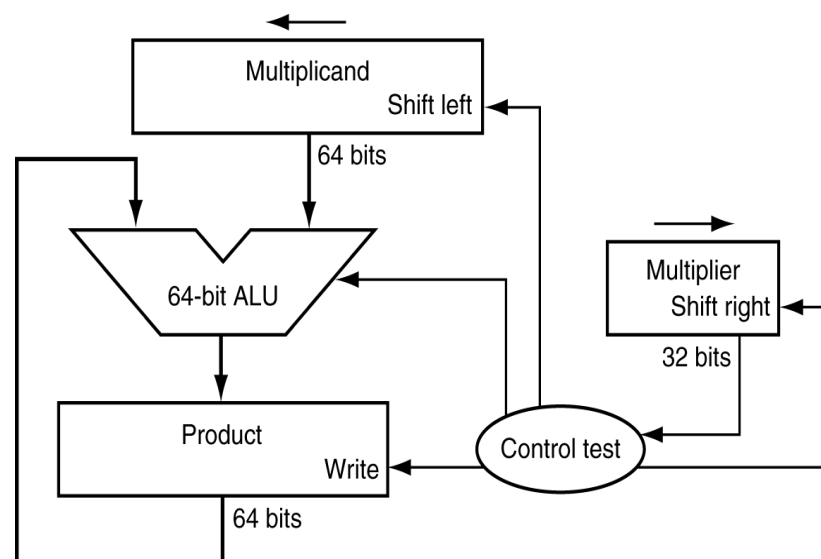
Length of product is the sum of operand lengths




Multiplication Algorithm (1st ver)

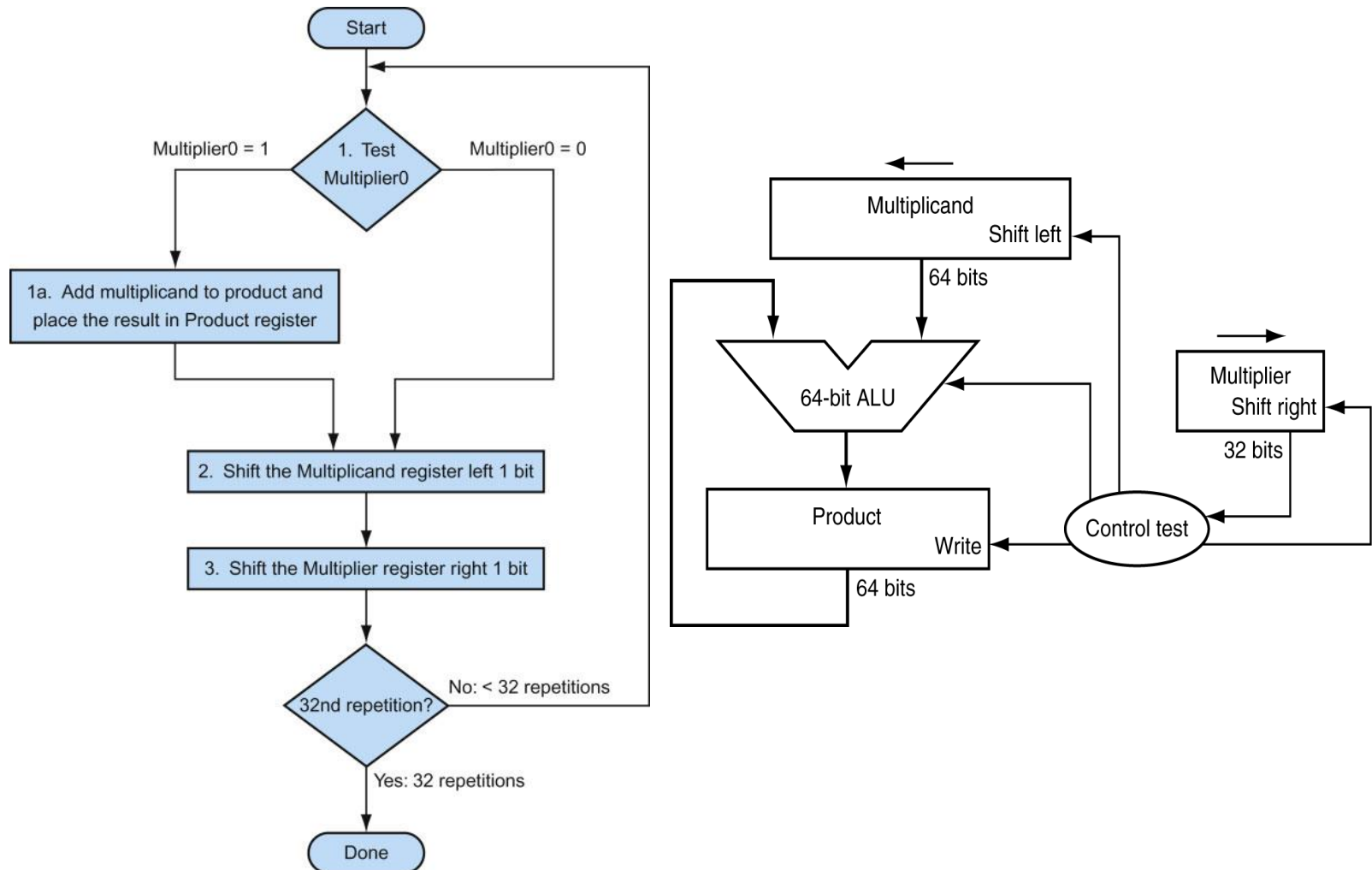


Multiplication (2nd ver)

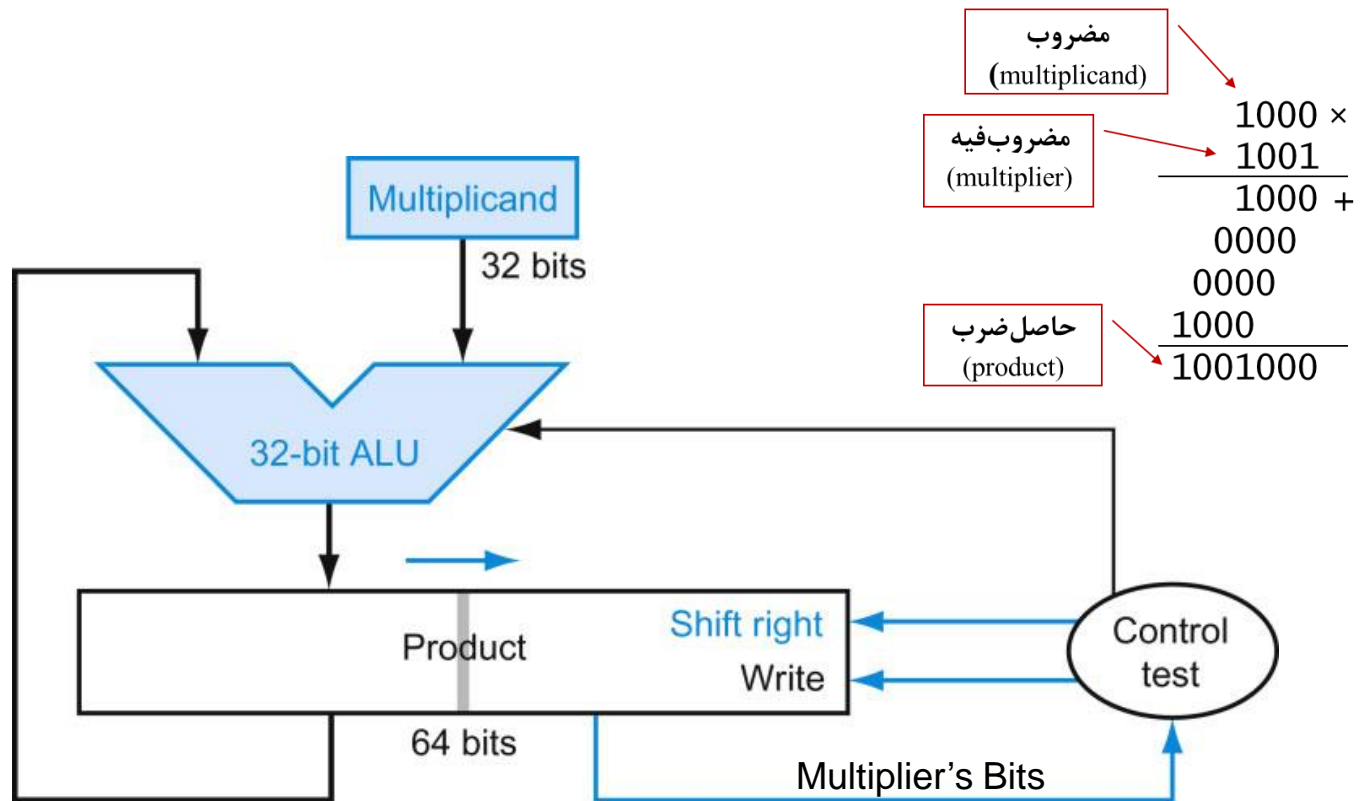

Combinational Multiplier


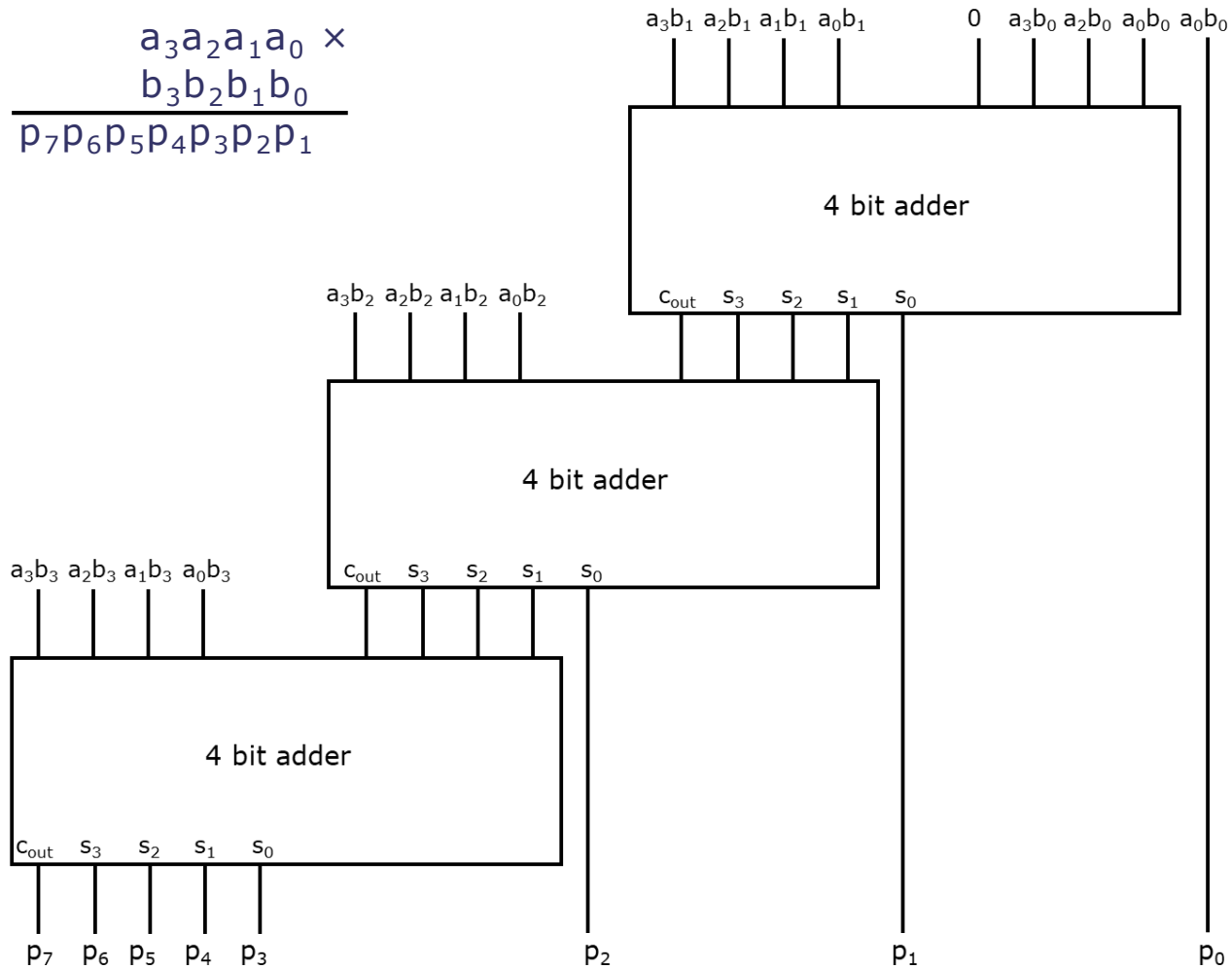


Combinational Multiplier (tree-form)

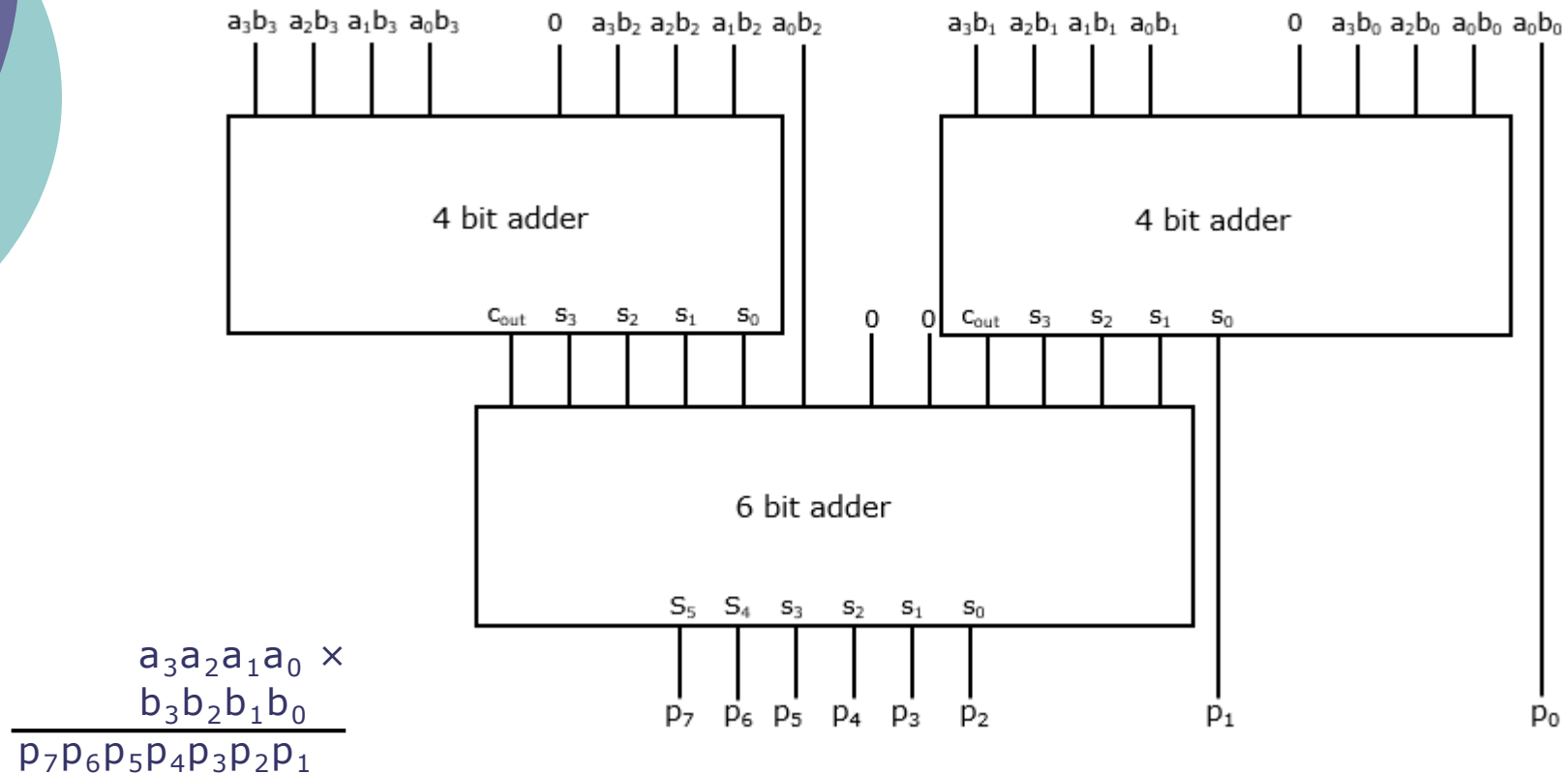



Addition of Multiple Numbers

Traditional Approach

 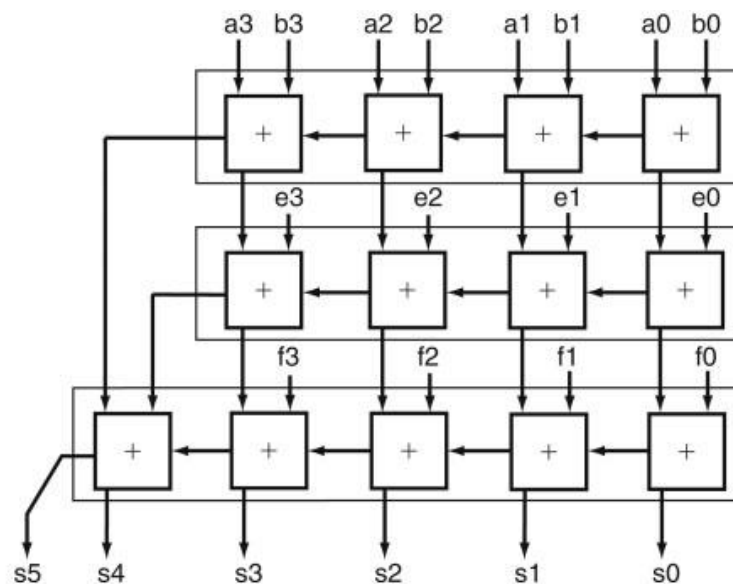


Addition of Multiple Numbers

Applying Carry Save Adders

 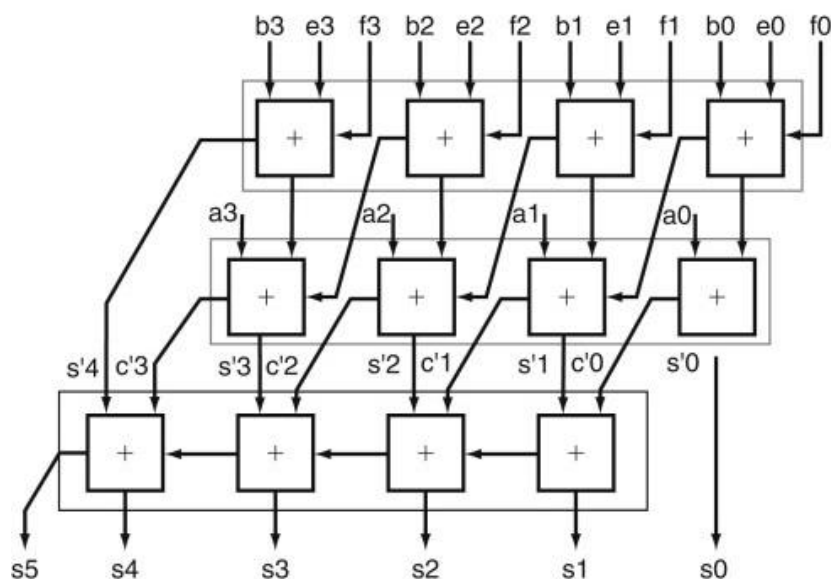

Carry-Save Adder Multiplier

 


Outlines

- Shift
- Addition/Subtraction
 - Ripple-Carry Adders
 - Carry Look-ahead Adders
 - Carry-Select Adders
- Multiplication
 - Shift-Add Multiplier
 - Combinational Multiplier
 - Carry-Save Adder Multiplier
- **Division**
- Floating Point
 - Representation
 - Arithmetic



Division

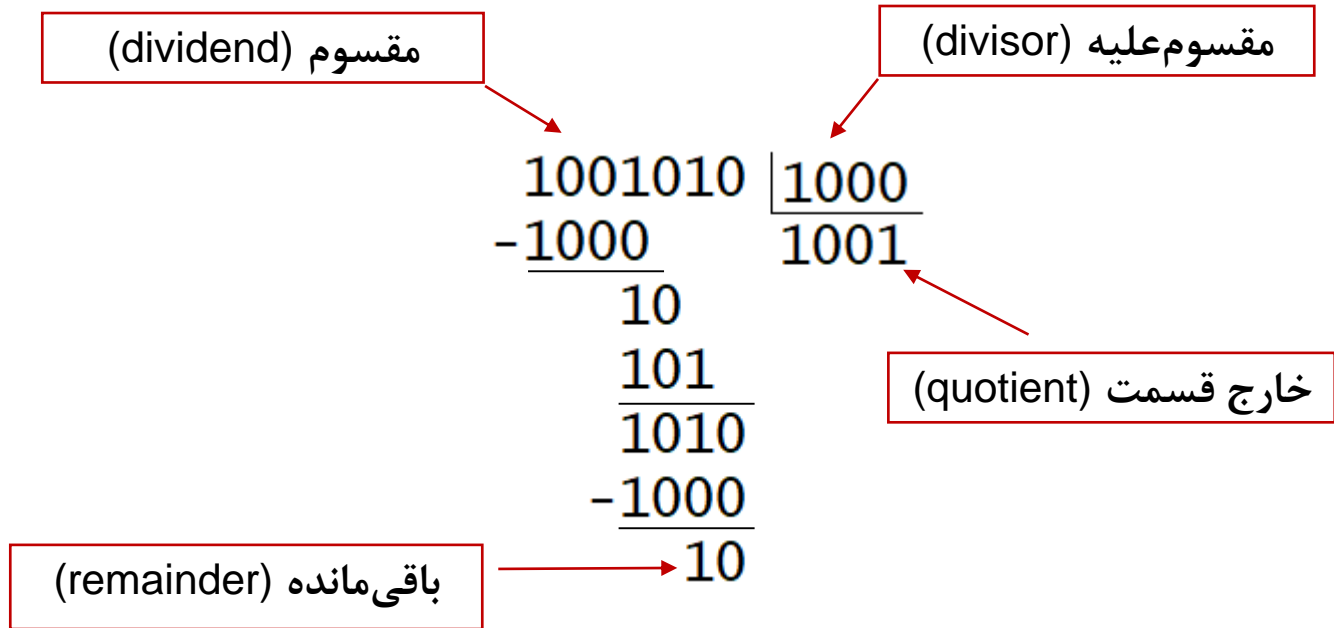



$$Dividend = Quotient \times Divisor + Remainder$$

$$|Remainder| < |Divisor|$$




Division Algorithm
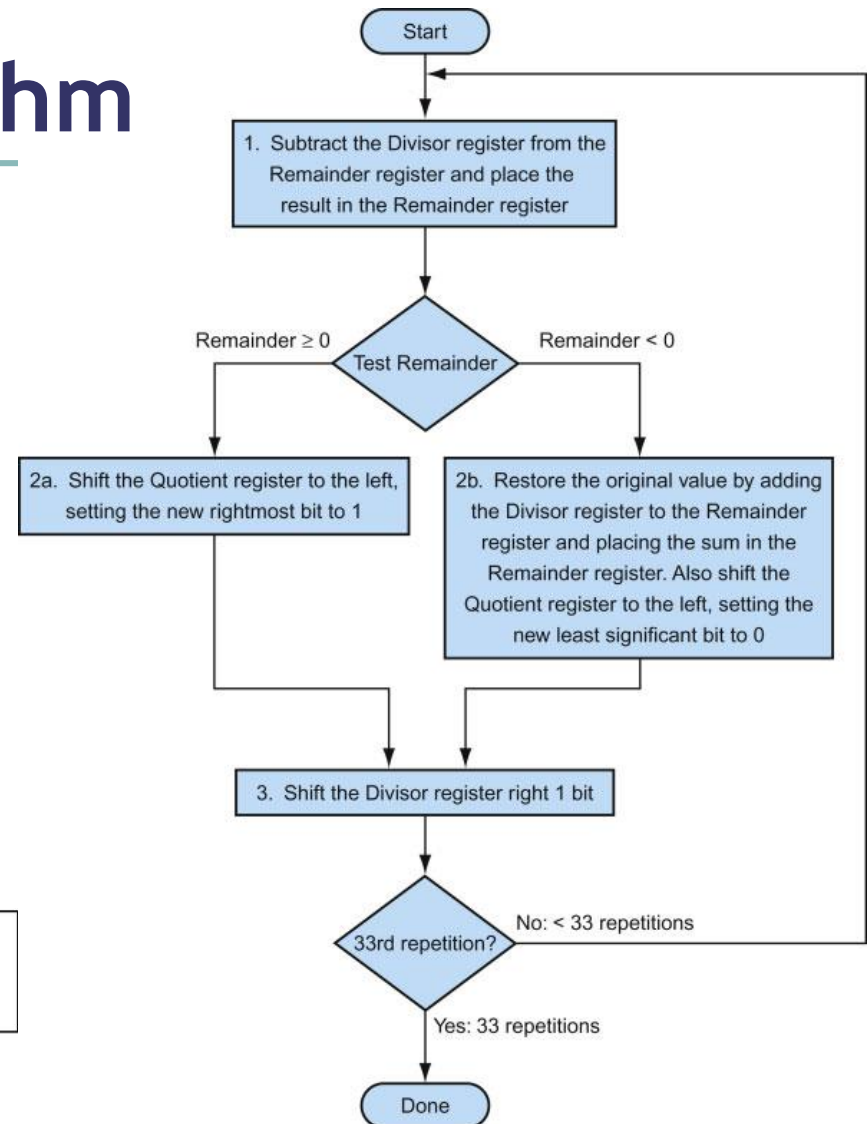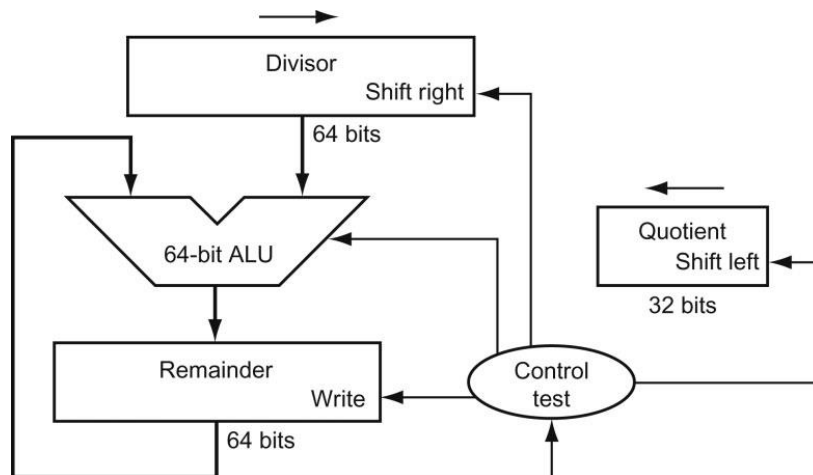
$$\begin{array}{r}
 1001010 \overline{) 1000} \\
 \underline{-1000} \\
 10 \\
 \underline{101} \\
 1010 \\
 \underline{-1000} \\
 10
 \end{array}$$



Division Algorithm (improved)

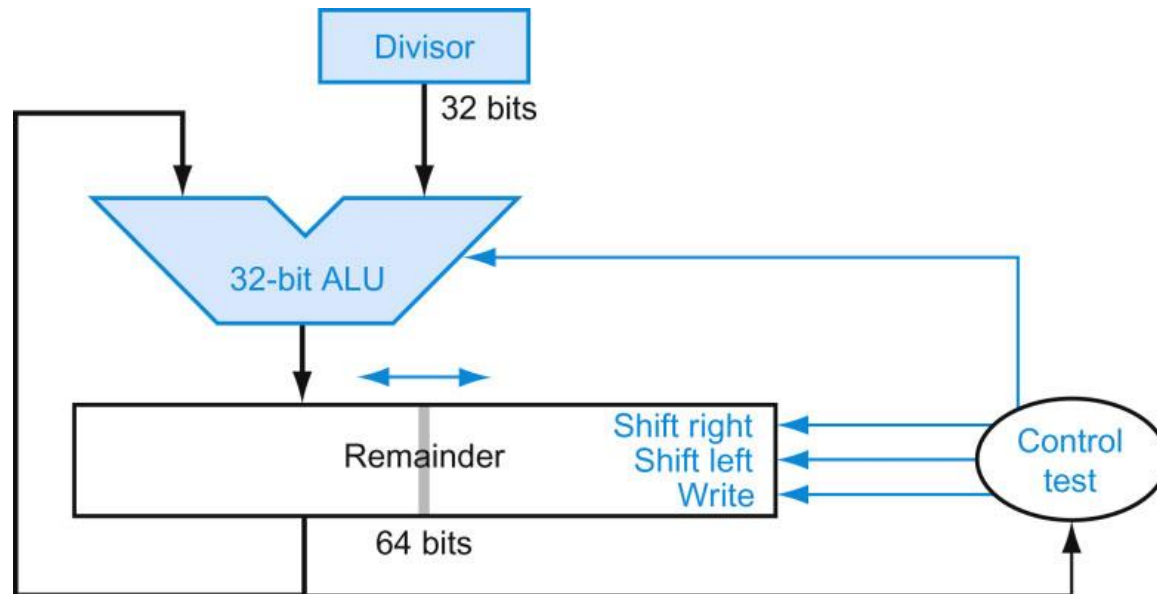

The Divisor register, ALU, and Quotient register are all 32 bits wide.


The ALU and Divisor registers are halved and the remainder is shifted left.

The Quotient register is combined with the right half of the Remainder register.

The Remainder register should really be 65 bits to make sure the carry out of the adder is not lost.



Multiplication vs. Division

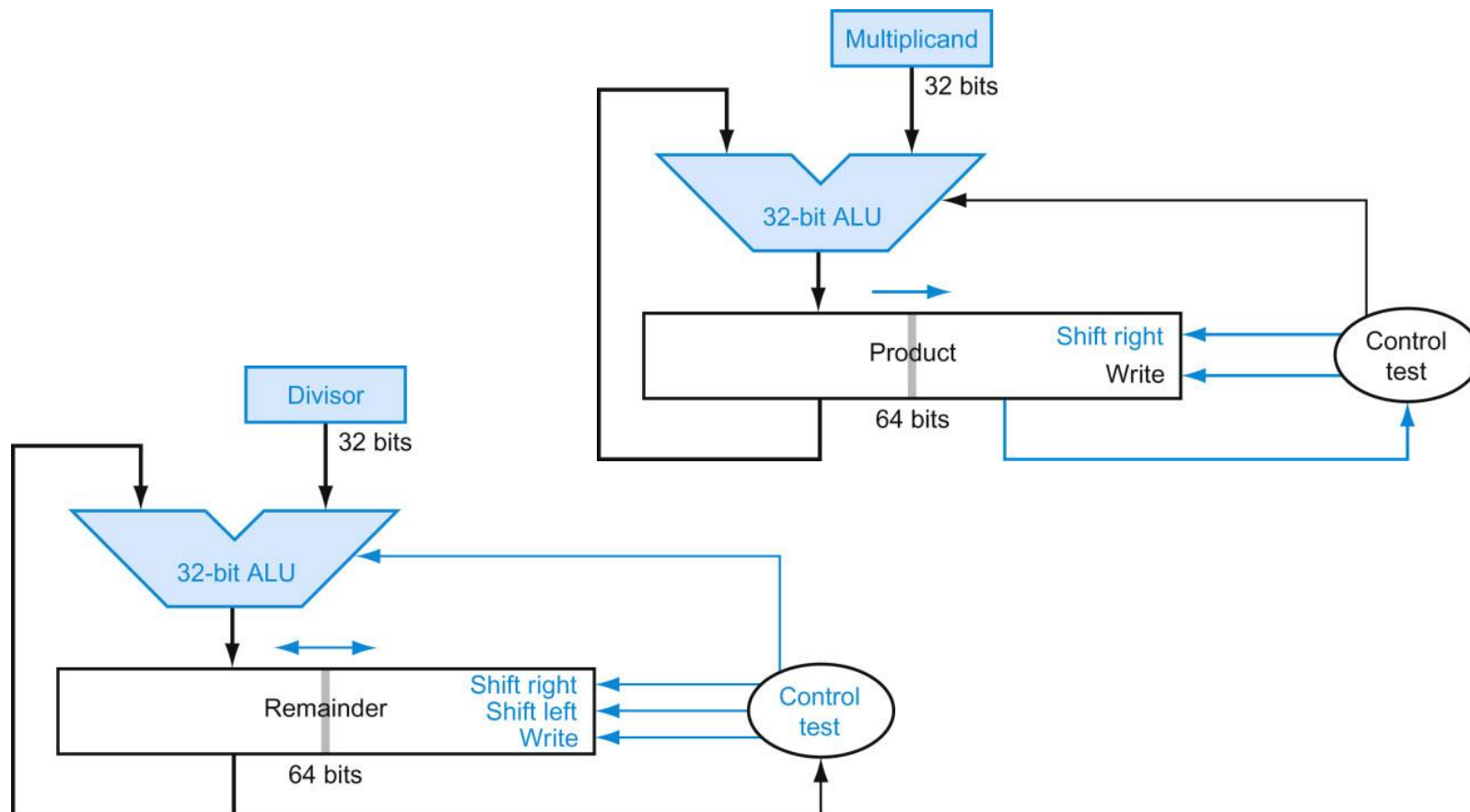

Signed Division

- Divide using absolute values, considering:
 - $\text{Dividend} = \text{Quotient} \times \text{Divisor} + \text{Remainder}$
- Adjust sign of quotient and remainder as required
 - no change in the absolute value of quotient
 - the **dividend** and **remainder** must have the **same signs**
 - e.g., divide ± 7 by ± 2



Fallacy

- Just as a **left shift** instruction can replace an integer **multiply** by a power of 2, a **right shift** is the same as an integer **division** by a power of 2
 - Only true for **unsigned** integers
 - Even with arithmetic right shift
 - e.g., try to shift right -5 twice



Outlines


- Shift
- Addition/Subtraction
 - Ripple-Carry Adders
 - Carry Look-ahead Adders
 - Carry-Select Adders
- Multiplication
 - Shift-Add Multiplier
 - Combinational Multiplier
 - Carry-Save Adder Multiplier
- Division
- Floating Point
 - Representation
 - Arithmetic



Real Numbers

○ Numbers with Fractions:

 - 3.14159...
- 2.17
- 0.0000001
- 12.5×10^{-12}
- $1.43 \times 10^{+12}$



○ Representation in computers:

- Fixed point
- Floating point



Fixed-Point Representation

○ A real Example:

- $d_{23}d_{22}...d_1d_0.f_{-1}f_{-2}f_{-3}f_{-4}f_{-5}f_{-6}f_{-7}f_{-8}$
- 24-bit: integer bits
- 8-bit: fraction bits

○ Application

- Used in CPUs with no floating-point unit
 - Embedded microprocessors and microcontrollers
- Digital Signal Processing (DSP) applications



Fixed-Point Representation (cont.)

- Consider 5-Bit Representation
 - $d_2d_1d_0.f_{-1}f_{-2}$
 - $(d_2 \times 2^2) + (d_1 \times 2^1) + (d_0 \times 2^0) + (f_{-1} \times 2^{-1}) + (f_{-2} \times 2^{-2})$
- Largest positive number?
- Smallest positive number?
- Largest magnitude negative number?
- Smallest magnitude negative number?



Fixed-Point Representation (cont.)

○ Arithmetic:

- $011.11 + 011.11 = 111.10$

out of range
(overflow)

- $010.10 \times 000.10 = 000001.0100$

out of range
(underflow)

- $000.01 \times 000.01 = 000000.0001$

- $011.01 \times 011.01 = ?$



Fixed-Point Representation (cont.)

○ Arithmetic:

- $011.11 + 011.11 = 111.10$

out of range
(overflow)

- $010.10 \times 000.10 = 000001.0100$

out of range
(underflow)

- $000.01 \times 000.01 = 000000.0001$

- $011.01 \times 011.01 = 001010.1001$

Both
overflow &
underflow



Fixed-Point Representation (cont.)

😊 Pros


- Simple hardware
- Fast computation
- **Different** precisions at different applications
 - 24bits/8bits , 18bits/12bits, 8bits/24bits

😞 Cons

- Low precision
- Small range



Scientific Notation (Decimal)

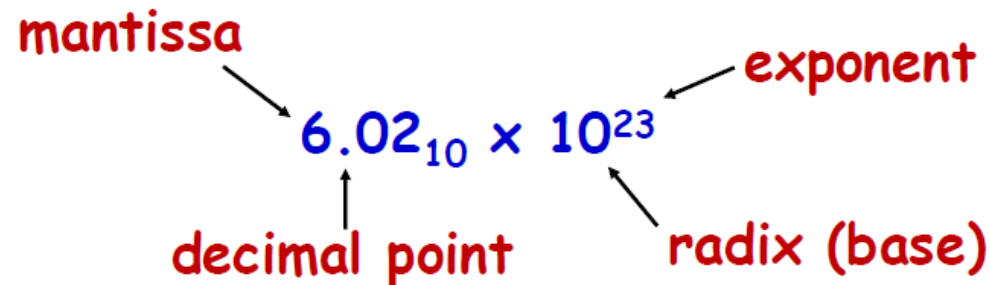

○ Normalized Form:

- Exactly one non-zero digit to left of decimal point

○ Alternatives to representing 0.0000000012:

- Normalized: 1.2×10^{-9}
- Not normalized: 0.12×10^{-8} , 12.0×10^{-10}



Normalized Scientific Notation (Binary)

fraction **exponent**

$$1.xxxx_{\text{two}} \times 2^{yyy}$$

binary point **radix (base)**

The diagram illustrates the components of normalized binary scientific notation. The expression is $1.xxxx_{\text{two}} \times 2^{yyy}$. The word 'fraction' is in red and has an arrow pointing to the 'xxxx' part of the mantissa. The word 'exponent' is in red and has an arrow pointing to the 'yyy' part of the exponent. The word 'binary point' is in red and has an arrow pointing to the decimal point between '1' and 'xxxx'. The word 'radix (base)' is in red and has an arrow pointing to the '2' in the base of the exponent.



Floating-Point Notation


- Floating Point Notation Consists of:
 - Fraction (F): 23 bits
 - Exponent (E): 8 bits
 - Fraction Sign bit (S)
 - Also called, **single precision** floating-point
- $N = (-1)^S \times (1+F) \times 2^E$

31	30	...	24	23	22	21	...	1	0
S	Exponent				Fraction				



Floating-Point Notation (cont.)

 - Pros (compared to fixed-point)
 - Very Wide Range
 - More precision bits
- Cons (compared to fixed-point)
 - Arithmetic operation more complicated
 - HW more complicated



Floating-Point Notation (cont.)

- $N = (-1)^S \times (1 + F) \times 2^E$
- Precision versus Range
 - More precision → smaller range?
 - Wider range → less precision?
- True for fixed-point
 - Not necessarily correct for floating point

31	30	...	24	23	22	21	...	1	0
S	Exponent				Fraction				



Floating-Point Notation (cont.)


- Overflow:
 - Exponent too large to fit in “Exponent” field
- Underflow:
 - Non-zero fraction so small to represent
 - Negative exponent too large to fit

31	30	...	24	23	22	21	...	1	0
S	Exponent				Fraction				



IEEE 754 Floating Point Standard

- There are many reasonable ways to represent floating-point numbers
- For many years, computer manufacturers used incompatible floating-point formats
- Results from one computer could not directly be interpreted by another computer.
- The Institute of Electrical and Electronics Engineers solved this problem by defining the **IEEE 754** floating point standard in 1985 defining floating-point numbers
- This floating-point format is now almost universally used

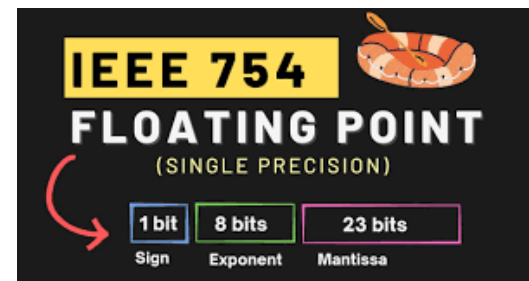

IEEE 754 - Single Precision

- **Signed-magnitude** notation for mantissa
- **Biased** (Excess $2^{n-1}-1$) notation for exponent

- $E_{\min} = 00000001$

- $E_{\max} = 11111110$

- $E = 00000000$ reserved for **zero**

- $E = 11111111$ reserved for **infinity** & **NaN**

- Smallest positive no: $1.17549435 \times 10^{-38}$

- Largest positive no: 3.4028235×10^{38}

31	30	...	24	23	22	21	...	1	0
S		Exponent						Fraction	

$$N = (-1)^S * (1 + F) * 2^{E-\text{bias}}$$



IEEE 754 - Double Precision

- Two words long (64 bits)
- Reduced chances of overflow/underflow
- Format
 - Sign bit (S)
 - Fraction (F): 52 bits
 - Exponent (E): 11 bits
- A bias of 1023 in Exponential part



More on IEEE 754 Standard

- Single precision (32bits)/Double precision (64bits)
- Normalized/ Denormalized forms
- Standard definitions for **zero**, **infinity**, **NaN**
- Check: <https://www.h-schmidt.net/FloatConverter/IEEE754.html>

Single precision		Double precision		Object represented
Exponent	Fraction	Exponent	Fraction	
0	0	0	0	0
0	Nonzero	0	Nonzero	\pm denormalized number
1–254	Anything	1–2046	Anything	\pm floating-point number
255	0	2047	0	\pm infinity
255	Nonzero	2047	Nonzero	NaN (Not a Number)



Denormalized Forms

- An attempt to squeeze every last bit of precision from a floating-point operation
- The smallest positive single precision normalized no:
 - $1.000000000000000000000000 \times 2^{-126}$
- The smallest single precision denormalized no:
 - $0.000000000000000000000001 \times 2^{-126} = 1.0 \times 2^{-149}$

31	30	...	24	23	22	21	...	1	0
S	Exponent				Fraction				



Floating-Point Addition

- 1 Align binary points
 - Shift number with smaller exponent (why?)
- 2 Add significands
- 3 Normalize result & check for over/underflow
- 4 Round and renormalize if necessary



Example


- Consider $0.5 + (-0.4375)$
 - $1.000_2 \times 2^{-1} + -1.110_2 \times 2^{-2}$
- 1 Align binary points (Shift number with smaller exponent)
 - $1.000_2 \times 2^{-1} + -0.111_2 \times 2^{-1}$
- 2 Add significands
 - $1.000_2 \times 2^{-1} + -0.111_2 \times 2^{-1} = 0.001_2 \times 2^{-1}$
- 3 Normalize result & check for over/underflow
 - $1.000_2 \times 2^{-4}$, with no over/underflow
- 4 Round and renormalize if necessary
 - $1.000_2 \times 2^{-4}$ (no change) = 0.0625



FP Adder Hardware

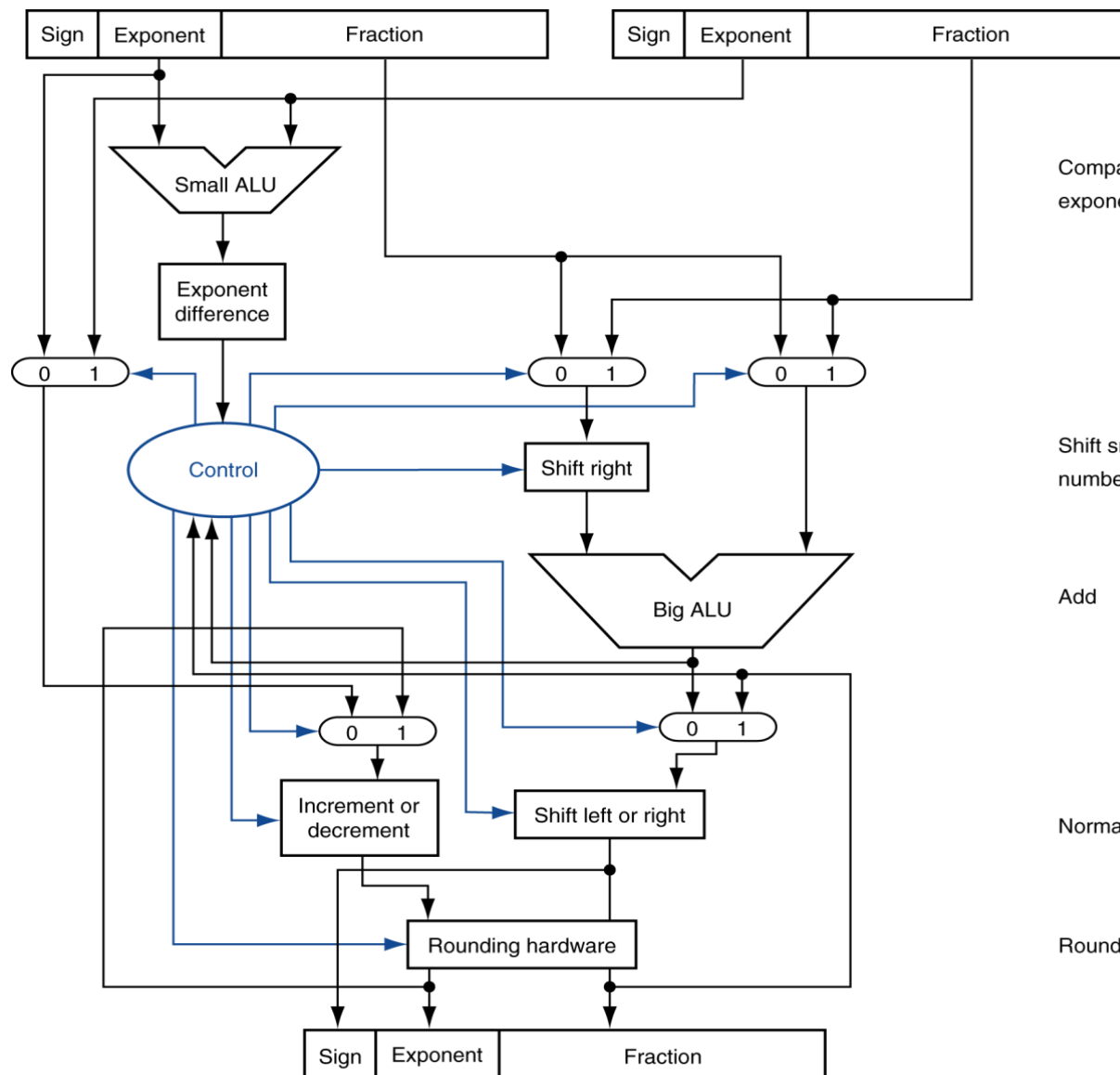- Much more complex than integer adder
- Doing it in one clock cycle takes too long
 - Much longer than integer operations
 - Slower clock would penalize all instructions
- FP adder usually takes several cycles
 - Can be pipelined





Compare exponents

Shift smaller number right

Add

Normalize

Round

1

2

3

4



Floating-Point Multiplication

- 1 Add exponents
 - For biased exponents, subtract bias from sum
- 2 Multiply significands
- 3 Normalize result & check for over/underflow
- 4 Round and renormalize if necessary
- 5 Determine sign of result from signs of operands



Example

- Consider $0.5 \times (-0.4375)$

- $1.000_2 \times 2^{-1} \times -1.110_2 \times 2^{-2}$

1 Add exponents

- Biased: $(-1 + 127) + (-2 + 127) = -3 + 254 - 127 = -3 + 127$

2 Multiply significands

- $1.000_2 \times 1.110_2 = 1.110_2 \Rightarrow 1.110_2 \times 2^{-3}$

3 Normalize result & check for over/underflow

- $1.110_2 \times 2^{-3}$, with no over/underflow

4 Round and renormalize if necessary

- $1.110_2 \times 2^{-3} = 0.21875$

5 Determine sign of result from signs of operands

- $-1.110_2 \times 2^{-3} = -0.21875$



FP Arithmetic Hardware

- FP multiplier is of similar complexity to FP adder
 - Uses a multiplier for significands instead of adder
- FP arithmetic hardware usually does
 - Addition, subtraction, multiplication, division, reciprocal, square-root, $FP \leftrightarrow integer$ conversion
- Operations usually takes several cycles
 - Can be pipelined



Concluding Remarks

- Bits have no inherent meaning
 - Interpretation depends on the operations applied
- Computer representations of numbers
 - Finite range and precision
 - Need to account for this in programs
- Bounded range and precision
 - Operations can overflow and underflow

