

Computer Architecture: Basic Arithmetic

Hossein Asadi (asadi@sharif.edu)

Department of Computer Engineering

Sharif University of Technology

Spring 2024



Copyright Notice

- Some Parts (text & figures) of this Lecture adopted from following:
 - Computer Organization & Design, The Hardware/Software Interface, 3rd Edition, by D. Patterson and J. Hennessey, MK publishing, 2005.
 - “Intro to Computer Architecture” handouts, by Prof. Hoe, CMU, Spring 2009.
 - “Computer Architecture & Engineering” handouts, by Prof. Kubiatowicz, UC Berkeley, Spring 2004.
 - “Intro to Computer Architecture” handouts, by Prof. Hoe, UWisc, Spring 2021.
 - “Computer Arch I” handouts, by Prof. Garzarán, UIUC, Spring 2009.
 - “Intro to Computer Organization” handouts, by Prof. Mahlke & Prof. Narayanasamy, Winter 2008.



Our Lectur Today




Topics Covered Today

- **Adders**
 - Ripple carry
 - Carry select adder
 - Carry-look-ahead adder
- **Multipliers**
 - Combinational multiplier
 - Sequential multiplier
 - Booth multiplier



Unsigned Binary Addition

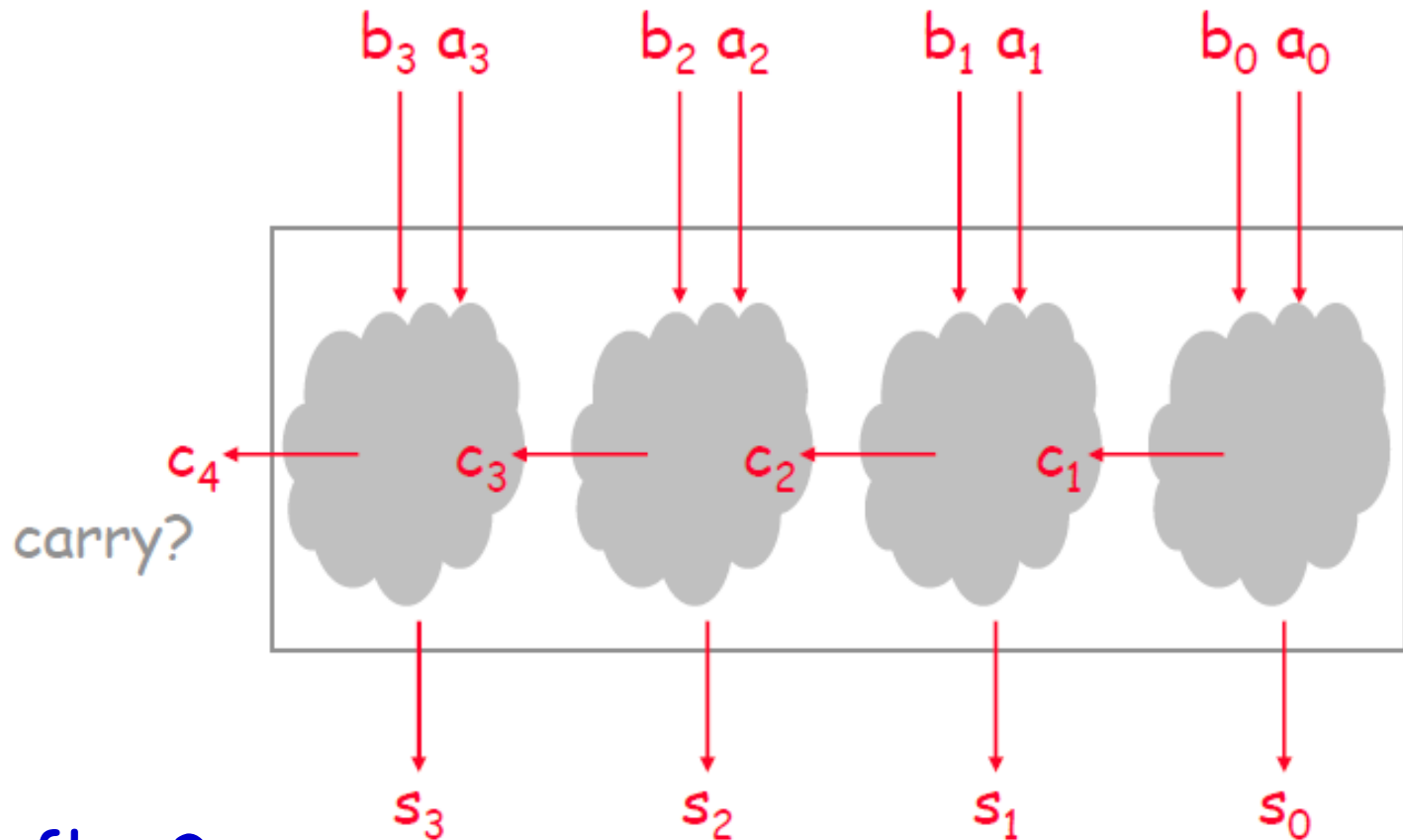


Overflow?

- Overflow = c_4



2's Complement Addition

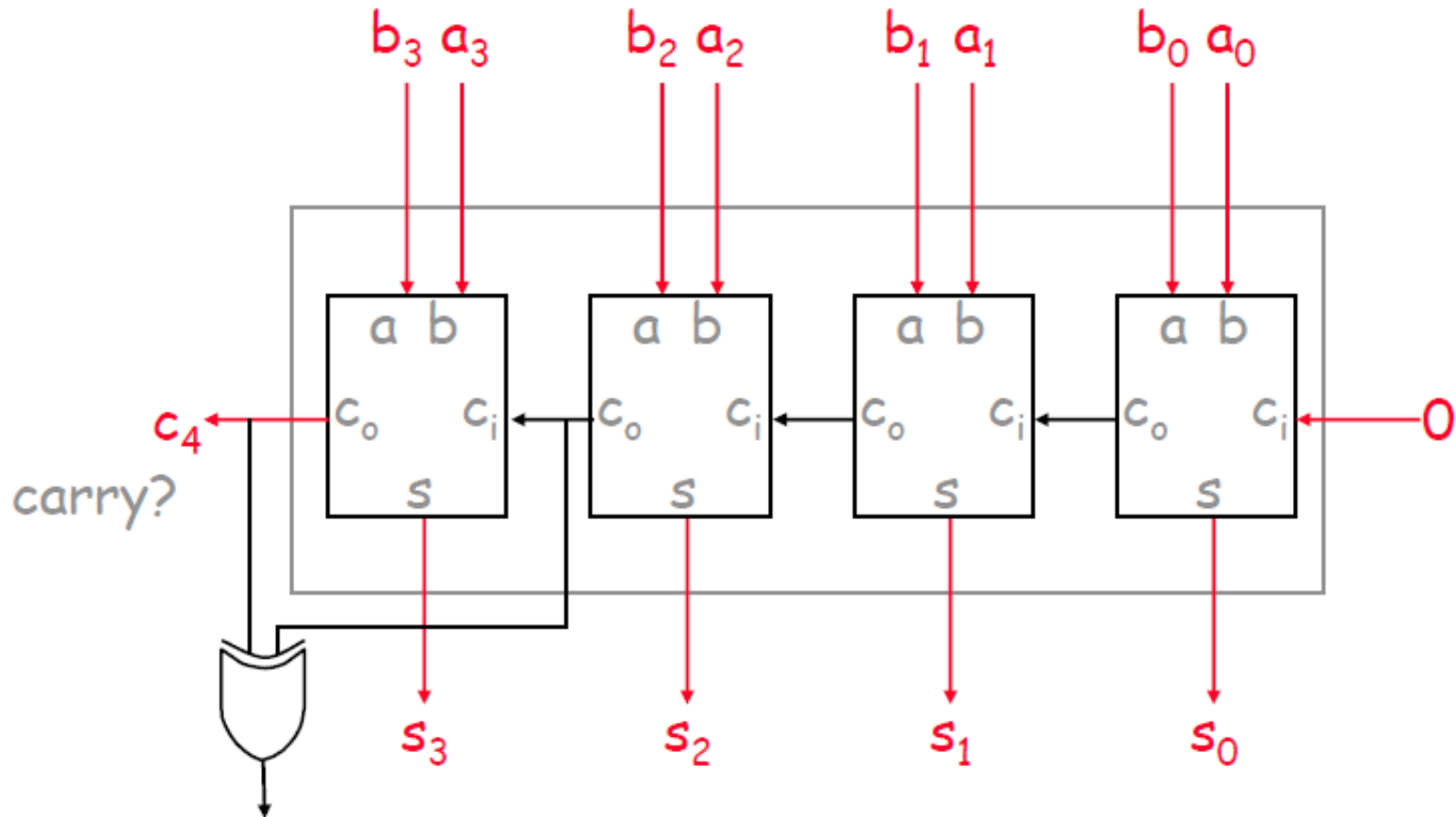


- $\text{Overflow} = (a_3 \text{ xor } b_3) ? 0 : (a_3 \text{ xor } s_3)$




2's Complement Subtraction

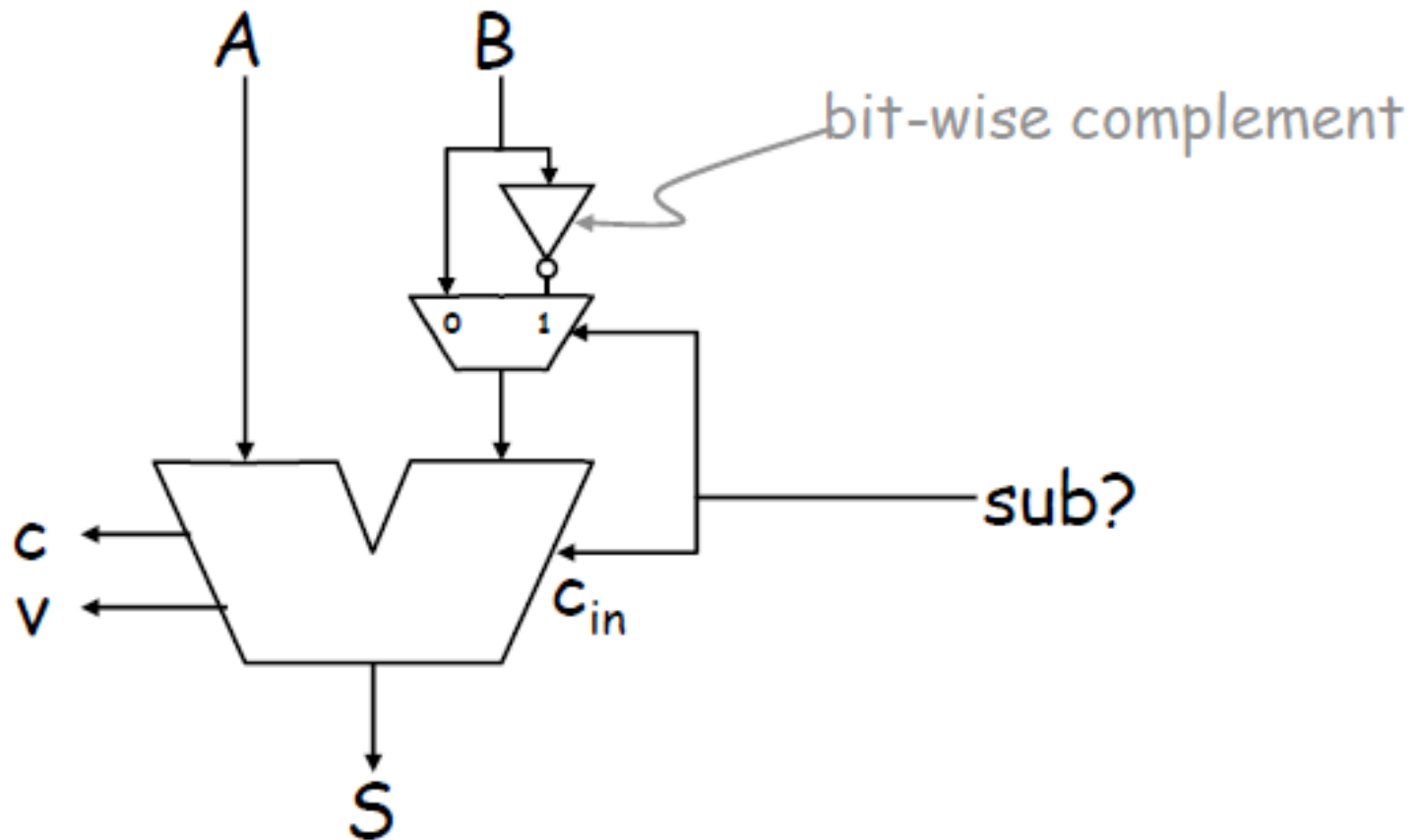- Subtraction
 - Similar to adding negative number



Analysis of an “n-bit” Ripple-Carry (RC) Adder

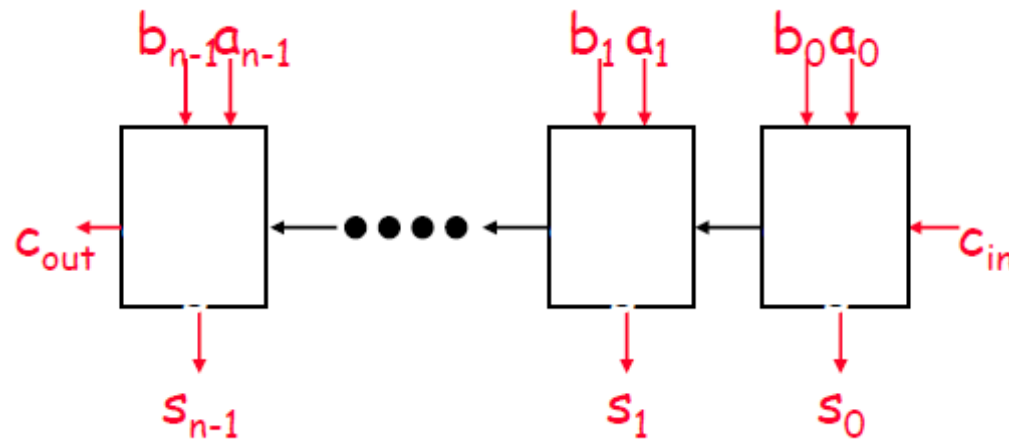- Size/Complexity
 - $n * \text{SizeOf(Full Adder)}$
 - $O(n)$
- Critical Path Delay
 - $n * \text{DelayOf(Full Adder)}$
 - $n * 2 * \text{gate delay}$
 - $O(n)$




High-Performance Adders

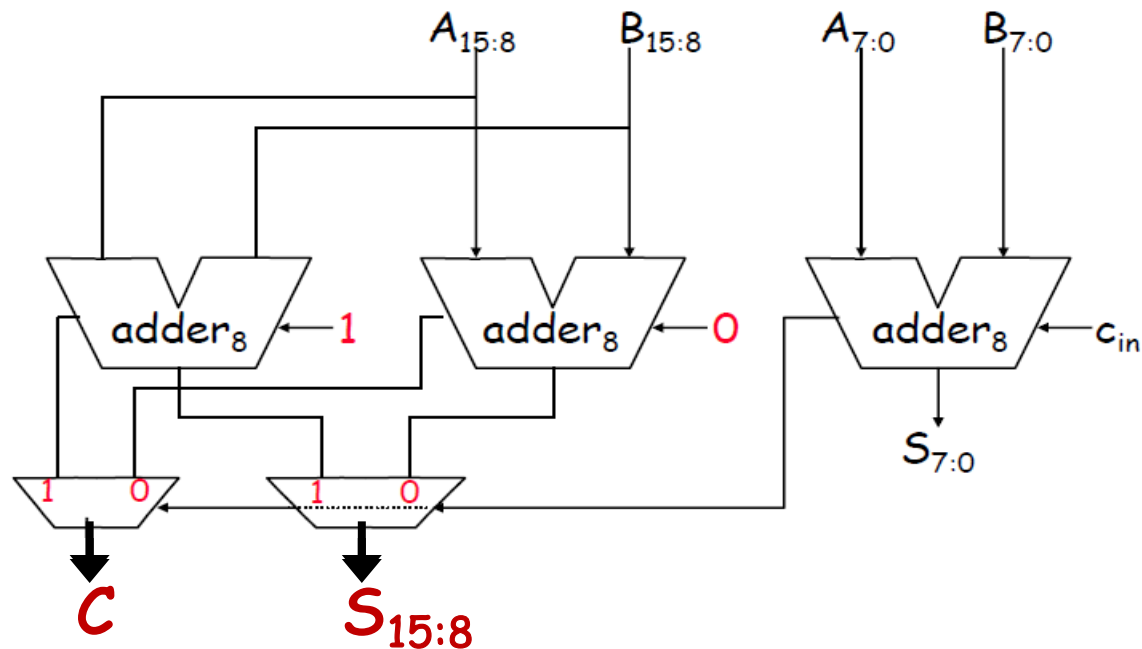- Question:
 - Any adder running faster than RC adder?
 - How to reduce carry propagation delay?
- Answer:
 - Compute intermediate carry signal
 - E.g., compute C_1 , C_2 , and C_3 in parallel




Carry-Select Adder (CSA)

- Delay
 - $8 \cdot D_{FA} + D_{mux}$
- Cost
 - $24 \cdot FA + Mux$



Multi-Stage CSA

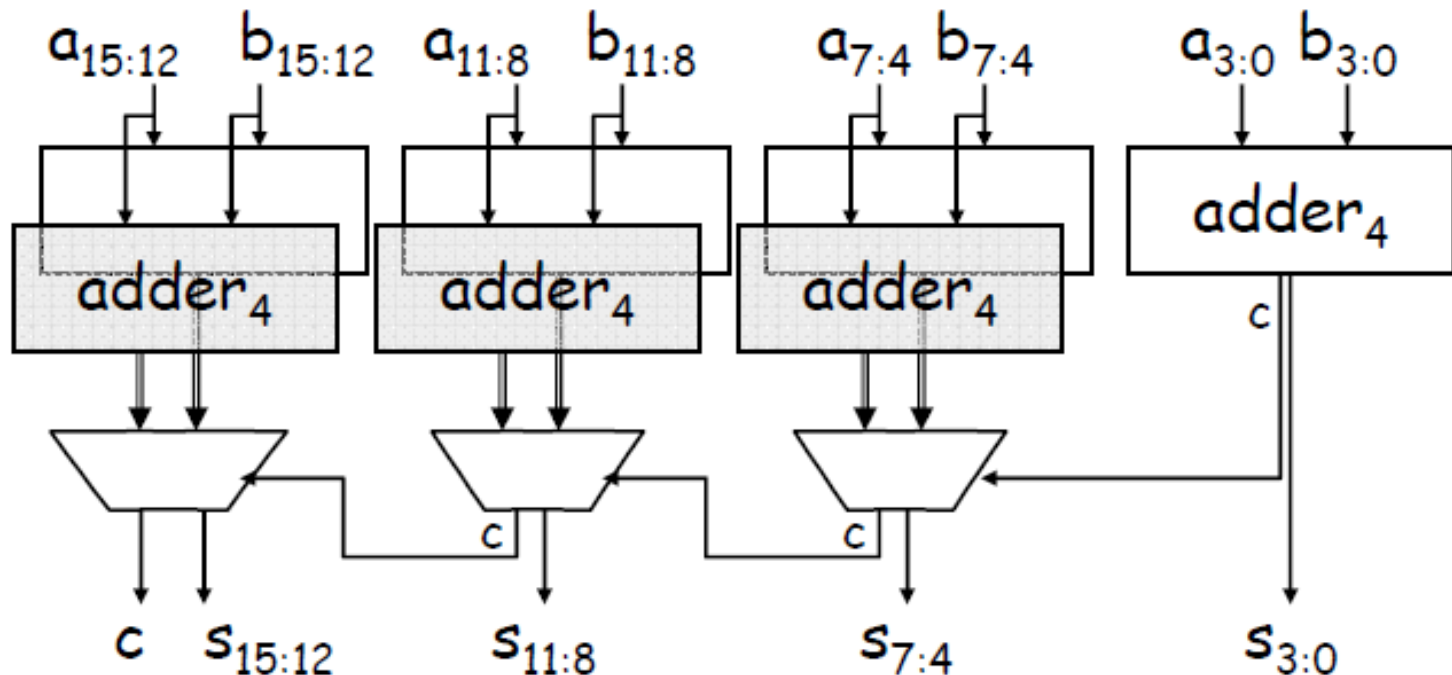- Delay
 - $4 \cdot D_{FA} + 3 \cdot D_{mux}$
- Cost
 - $28 \cdot FA + 3 \cdot Mux$



Multi-Stage CSA (cont.)

- K-Stage n-bit CSA
- Delay
 - $(n/k) \cdot D_{FA} + (k-1) \cdot D_{mux}$
- Cost
 - $N \cdot \{(2k-1)/k\} \cdot FA + (k-1) \cdot Mux$



Carry Generate & Propagate


- If $a.b = 1 \rightarrow C_{out} = 1$ regardless of C_{in}
 - Carry generate
- If $a \text{ xor } b = 1 \rightarrow C_{out} = C_{in}$
 - Carry propagate
- We define
 - $G_i = a_i.b_i$ (Generate)
 - $P_i = a_i \text{ xor } b_i$ (Propagate)
 - $\rightarrow C_{i+1} = G_i + P_i.C_i$



Carry Look-Ahead Adder

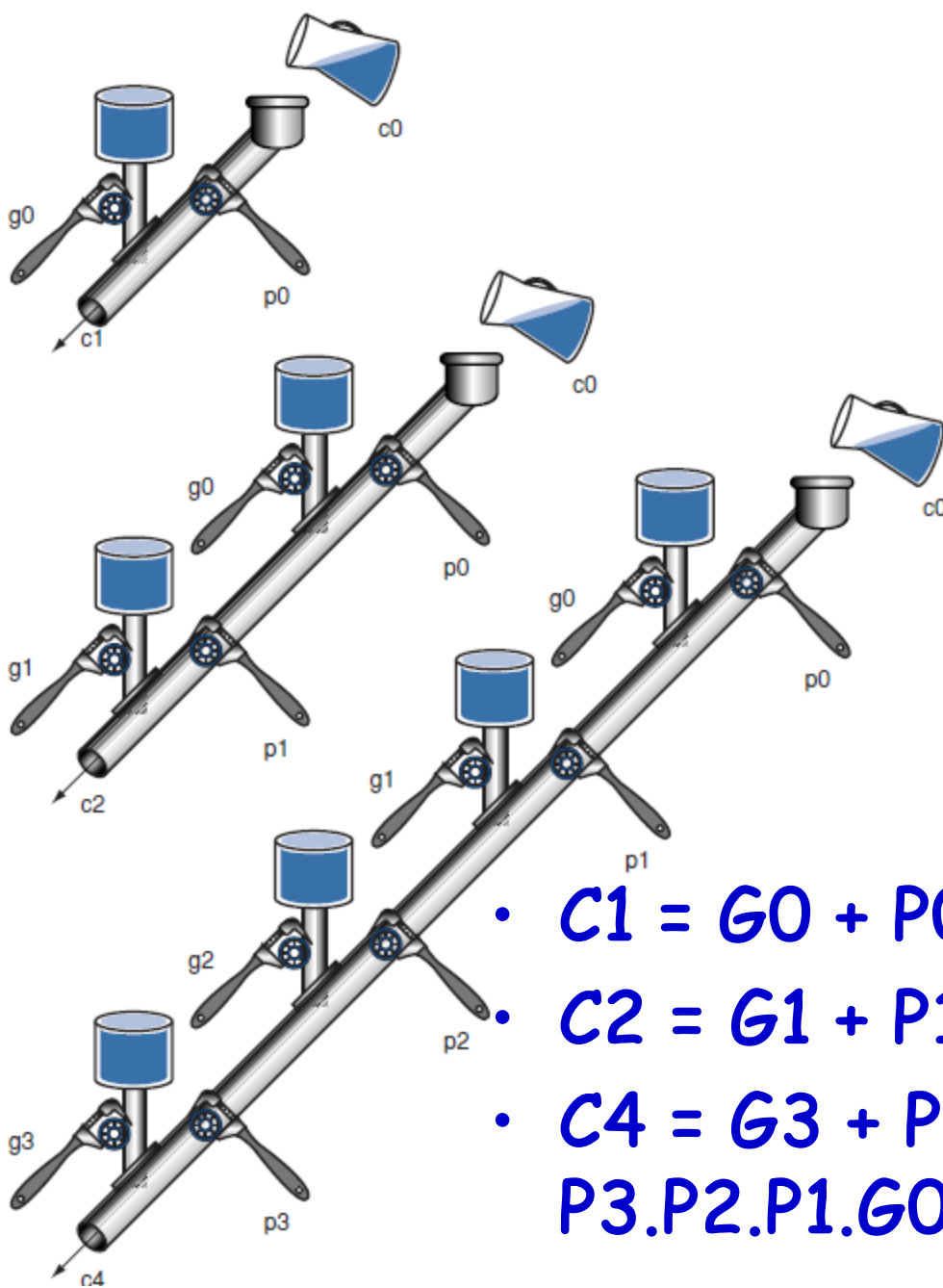- $C1 = G0 + P0.C0$
- $C2 = G1 + P1.C1 = G1 + P1.(G0+P0.C0)$
 $= G1 + P1.G0 + P1.P0.C0$
- $C3 = G2 + P2.G1 + P2.P1.G0 + P2.P1.P0.C0$
- $C4 = G3 + P3.G2 + P3.P2.G1 + P3.P2.P1.G0$
 $+ P3.P2.P1.P0.C0$





- $C1 = G0 + P0.C0$
- $C2 = G1 + P1.G0 + P1.P0.C0$
- $C4 = G3 + P3.G2 + P3.P2.G1 + P3.P2.P1.G0 + P3.P2.P1.P0.C0$

Carry Look-Ahead Adder (cont.)

- Delay Complexity
 - $O(\log n)$
- Size Complexity
 - $O(n^2)$
- Manageable for Small n 's
- Can be used in **Two-Level** CLA Adders
 - 16-bit adder using 4-bit CLA modules



Carry Look-Ahead Adder (cont.)

- Dg: Delay of a Single Gate
- At each Stage
 - Dg for generating all P_i and G_i
 - $2 \cdot D_g$ for generating all C_i (2-level gate)
 - $2 \cdot D_g$ for generating all S_i (2-level gate)
- Total Delay: $5 \cdot D_g$ (independent of n)
 - Issue?
 - $D(\text{gate with } f_{\text{ainin}}=32) \gg D(\text{gate w } f_{\text{ainin}}=2)$
 - [Copyright I. Kormen, umass, spring'08]



Carry Look-Ahead Adder (cont.)

- n Stages Divided into Groups
 - Separate CLA in each group
 - Group interconnected by RC
- Example: Group Size =4
 - Dg for generating all Pi and Gi
 - $2 \cdot Dg$ to propagate carry through a group
 - $(n/4) \cdot 2 \cdot Dg$ to propagate carry using RC
 - $2 \cdot Dg$ to generate Si
 - Total: $[2(n/4)+3]Dg = [n/2+3] \cdot Dg \rightarrow$
 - 75% reduction compared to full RC




Multiplier


- Combinational Multiplier
 - Also called array multiplier
- Shift-Add Multiplier
- Booth Multiplier



Combinational Multiplier

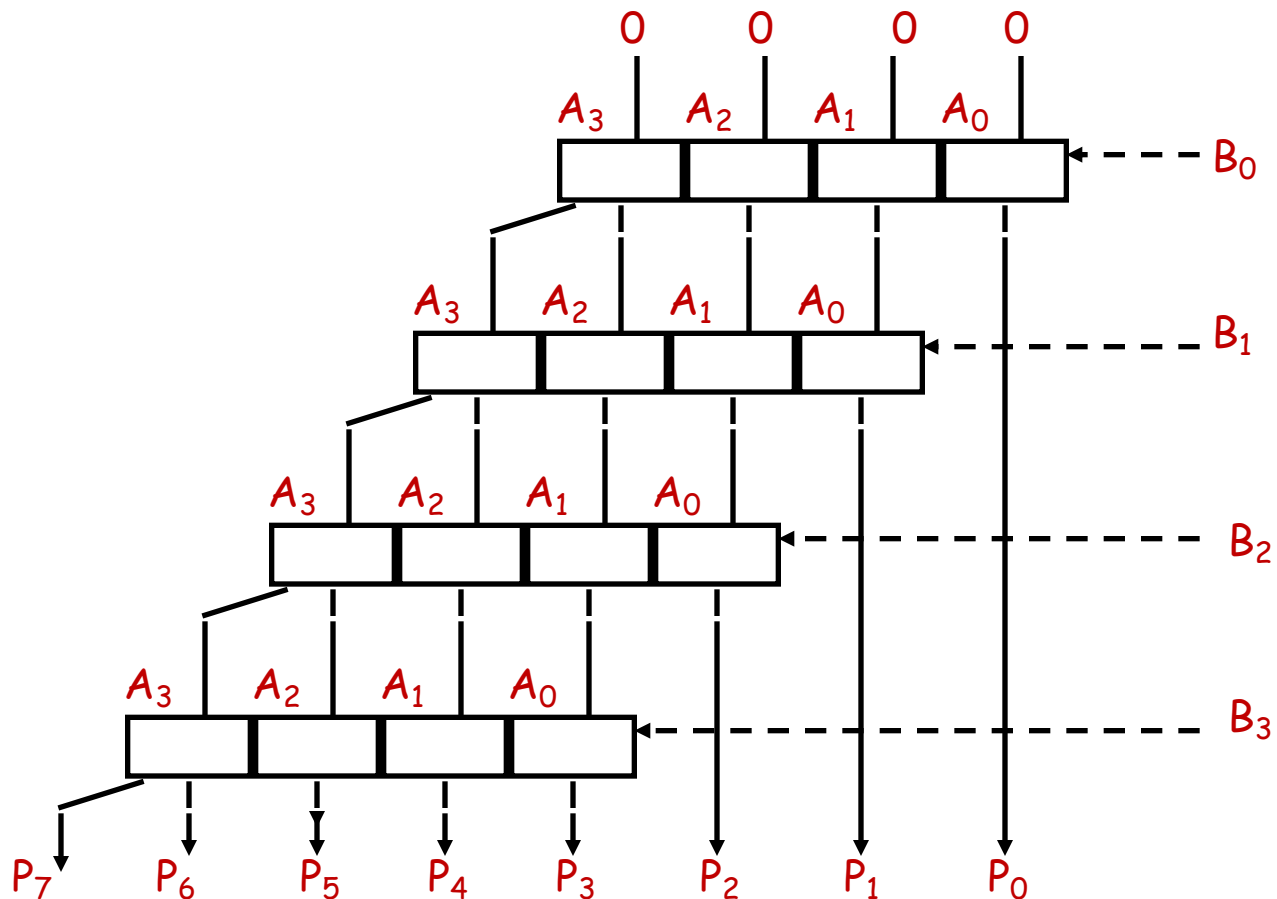

Shift-Add Multiplier

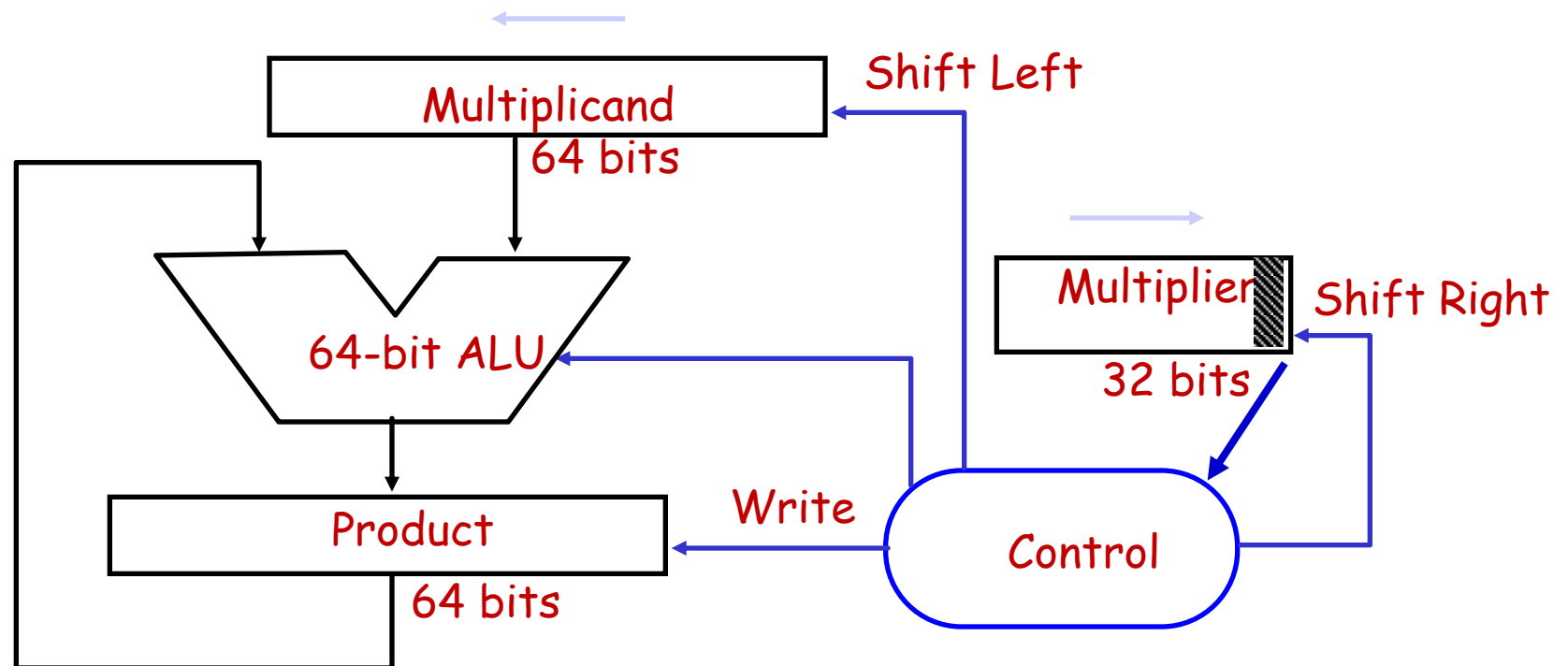

Booth's Algorithm

- Example $2 \times 6 = 0010 \times 0110$:

$$\begin{array}{r}
 0010 \\
 x 0110 \\
 \hline
 + 0000 \quad \text{shift (0 in multiplier)} \\
 + 0010 \quad \text{add (1 in multiplier)} \\
 + 0010 \quad \text{add (1 in multiplier)} \\
 + 0000 \quad \text{shift (0 in multiplier)} \\
 \hline
 00001100
 \end{array}$$

- ALU with add or subtract gets same result in more than one way:

$$6 = -2 + 8$$

$$0110 = -00010 + 01000 = 11110 + 01000$$

- For example

$$\begin{array}{r}
 0010 \\
 x 0110 \\
 \hline
 0000 \quad \text{shift (0 in multiplier)} \\
 - 0010 \quad \text{sub (first 1 in multiply)} \\
 0000 \quad \text{shift (mid string of 1s)} \\
 + 0010 \quad \text{add (prior step had last 1)} \\
 \hline
 00001100
 \end{array}$$



Booth's Algorithm (cont.)

Current Bit	Bit to Right	Explanation	Example	Op
1	0	Begins run of 1s	000111 <u>1</u> 000	sub
1	1	Middle of run of 1s	00011 <u>11</u> 000	none
0	1	End of run of 1s	00 <u>01</u> 111000	add
0	0	Middle of run of 0s	0 <u>00</u> 1111000	none

- Originally developed for Speed
 - When shift was faster than add



Booth Encoding: Example

1	0	0	1	1	1	1	0	1	0
-1	0	1	0	0	0	-1	1	-1	0



Booth's Algorithm: Example

- Example
 - multiply $(-5) \times 2$
- Let's use 5-bit 2's complement:
 - A: -5 is **11011** (multiplier)
 - B: 2 is **00010** (multiplicand)



Beginning Product

- Multiplier is:

11011

- Add 5 leading zeros to **multiplier** to get **beginning product**:

00000 11011



Step 1 for each pass

- Use **LSB** (least significant bit) and **previous LSB** to determine arithmetic action
 - If it is FIRST pass, use **0** as previous LSB
- Possible arithmetic actions:
 - **00** → no arithmetic operation
 - **01** → add multiplicand to left half of product
 - **10** → subtract multiplicand from left half of product
 - **11** → no arithmetic operation



Step 2 for Each Pass

- Perform an **arithmetic right shift** (ASR) on entire product
- Note:
 - For X-bit operands, Booth's algorithm requires X passes



Example

- Let's continue with our example of multiplying **(-5) x 2**
- Remember:
 - -5 is **11011** (multiplier)
 - 2 is **00010** (multiplicand)
- And we added 5 leading zeros to **multiplier** to get **beginning product**:

00000 11011



Example

- Initial Product and previous LSB

00000 11011 0

(Note: Since this is first pass, we use 0 for previous LSB)

- Pass 1, Step 1: Examine last 2 bits

00000 11011 0

Last two bits are 10, so we need to:

subtract **multiplicand** from left half of product



Example: Pass 1 (cont.)

- Pass 1, Step 1: Arithmetic action

$$\begin{array}{r} (1) \quad 00000 \quad \text{(left half of product)} \\ -00010 \quad \text{(multiplicand)} \\ \hline 11110 \quad \text{(uses a phantom borrow)} \end{array}$$

- Place result into **left half** of product

11110 11011 0



Example: Pass 1 (cont.)

- Pass 1, Step 2: ASR (arithmetic shift right)

– Before ASR

11110 11011 0

– After ASR

11111 01101 1

(left-most bit was 1, so a 1 was shifted in on the left)

- Pass 1 is complete



Example: Pass 2

- Current Product and **previous LSB**

11111 01101 1

- Pass 2, Step 1: Examine last 2 bits

11111 01101 1

Last two bits are **11**, so we do NOT need to perform an arithmetic action --

just proceed to step 2.



Example: Pass 2 (cont.)

- Pass 2, Step 2: ASR (arithmetic shift right)

– Before ASR

11111 01101 1

– After ASR

11111 10110 1

(left-most bit was 1, so a 1 was shifted in on left)

- Pass 2 is complete



Example: Pass 3

- Current Product and **previous LSB**

11111 10110 1

- Pass 3, Step 1: Examine last 2 bits

11111 10110 1

Last two bits are 01, so we need to:
add **multiplicand** to left half of product



Example: Pass 3 (cont.)

- Pass 3, Step 1: Arithmetic action

$$\begin{array}{rcl} (1) & 11111 & \text{(left half of product)} \\ & +00010 & \text{(multiplicand)} \\ \hline & 00001 & \text{(drop the leftmost carry)} \end{array}$$

- Place result into **left half** of product

00001 10110 1



Example: Pass 3 (cont.)

- Pass 3, Step 2: ASR (arithmetic shift right)

– Before ASR

00001 10110 1

– After ASR

00000 11011 0

(left-most bit was 0, so a 0 was shifted in on left)

- Pass 3 is complete



Example: Pass 4

- Current Product and **previous LSB**

00000 11011 0

- Pass 4, Step 1: Examine last 2 bits

00000 1101**1** **0**

Last two bits are **10**, so we need to:

subtract **multiplicand** from left half of product



Example: Pass 4 (cont.)

- Pass 4, Step 1: Arithmetic action

$$\begin{array}{r} (1) \quad 00000 \quad \text{(left half of product)} \\ -00010 \quad \text{(multiplicand)} \\ \hline 11110 \quad \text{(uses a phantom borrow)} \end{array}$$

- Place result into **left half** of product

11110 11011 0



Example: Pass 4 (cont.)

- Pass 4, Step 2: ASR (arithmetic shift right)

– Before ASR

11110 11011 0

– After ASR

11111 01101 1

(left-most bit was 1, so a 1 was shifted in on left)

- Pass 4 is complete

Example: Pass 5

- Current Product and **previous LSB**

11111 01101 1

- Pass 5, Step 1: Examine last 2 bits

11111 01101 1

The last two bits are **11**, so we do NOT need to perform an arithmetic action --
just proceed to step 2.



Example: Pass 5 (cont.)

- Pass 5, Step 2: ASR (arithmetic shift right)

– Before ASR

11111 01101 1

– After ASR

11111 10110 1

(left-most bit was 1, so a 1 was shifted in on left)

- Pass 5 is complete



Final Product

- We have completed 5 passes on 5-bit operands, so we are done.
- Dropping the **previous LSB**, resulting **final product** is:

11111 10110



Verification

- To confirm we have correct answer, convert the 2's complement **final product** back to decimal
- Final product: **11111 10110**
- Decimal value: **-10**

which is CORRECT product of:

$$(-5) \times 2$$





Thanks for Your Attention!

